




Dept. of Computer Science and Engineering
University of Rajshahi
www.ru.ac.bd
Dr. Shamim Ahmad

Combinatorial Circuit Design


- Some useful components can be designed using the gates and the components described so far during the course
- This presentation describes the design of a binary coded decimal (BCD) to 7 segment decoder, which is used in digital displays
- This design will use only combinatorial logic gates, making use of the minimization logic techniques we have described

Design Requirements

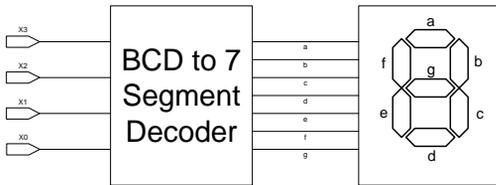


Design the logic circuitry that will drive a seven segment LED display and will be able to represent numbers from 0 to 9

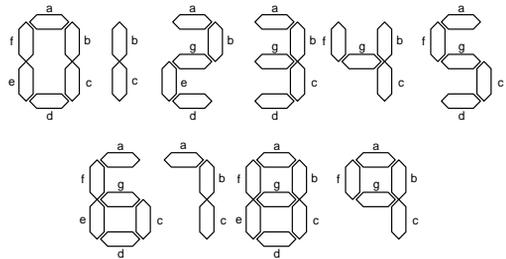Possible numbers and their representation on 7 segment display





Truth Table



X3	X2	X1	X0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0	x	x	x	x	x	x	x
1	0	1	1	x	x	x	x	x	x	x
1	1	0	0	x	x	x	x	x	x	x
1	1	0	1	x	x	x	x	x	x	x
1	1	1	0	x	x	x	x	x	x	x
1	1	1	1	x	x	x	x	x	x	x

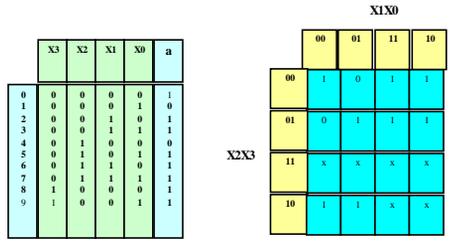


Signal a implementation

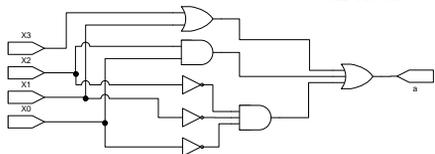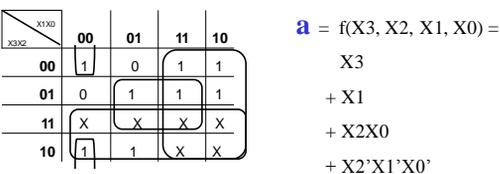


Signal b implementation

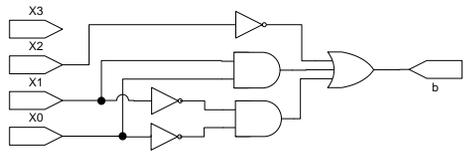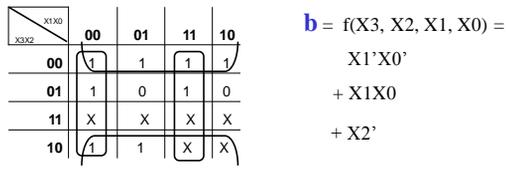


Signal **c** implementation

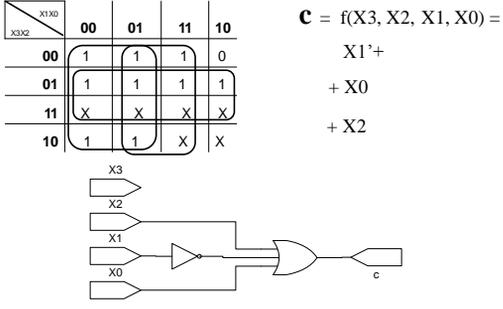


Signal **d** implementation

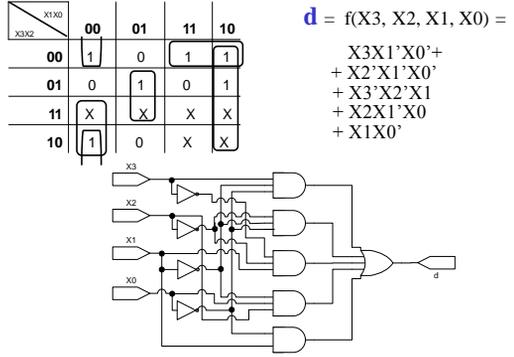


Signal **e** implementation

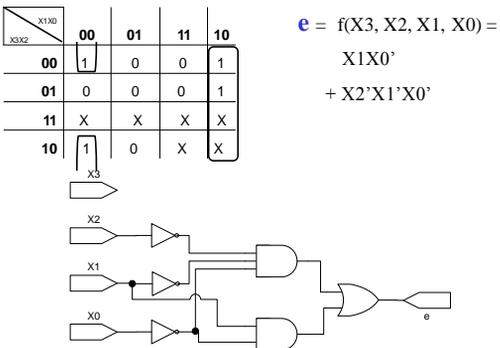


Signal **f** implementation

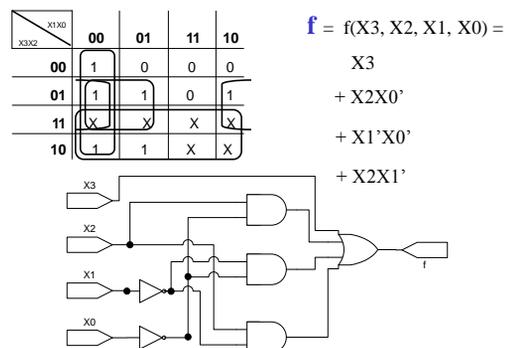

Signal g implementation

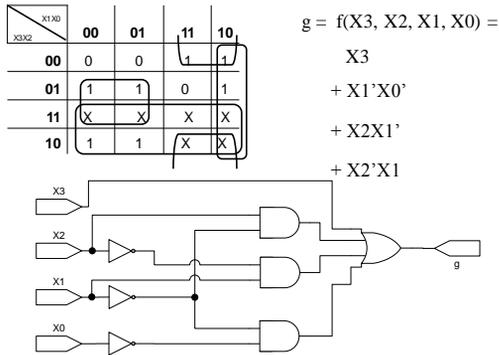


7 segment display

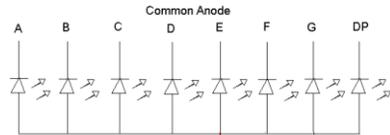


- All the **anode segments** are connected together
- **Power must** be applied externally to the **anode** connection that is common to all the segments
- By **applying the ground** to a particular segment (i.e. a,b,g etc.), the appropriate segment will light up

7 segment common anode

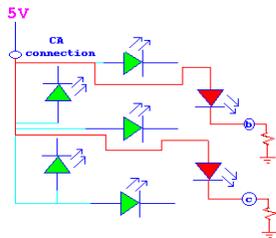


- **A resistor** should be added in order to limit the current through LED
- The current to light the active LED is sink by the logic component, which is preferable

7 segment Common Cathode

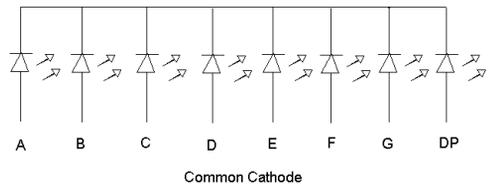

- All the **cathode of the LED** are connected together
- The **common connection must be grounded** and **power** must be applied to **appropriate segment** in order to illuminate that segment
- The current to light the active LED is generated by the logic component, which generates the logic 1

7447 TTL IC

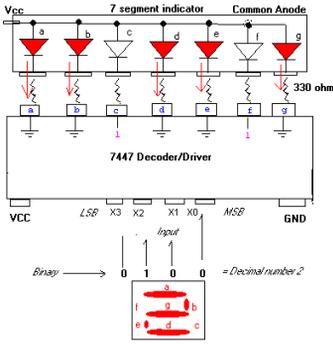

- Real world example of BCD to 7 segment decoder
- Outputs of the decoder are active low and a common anode 7 segment display is used