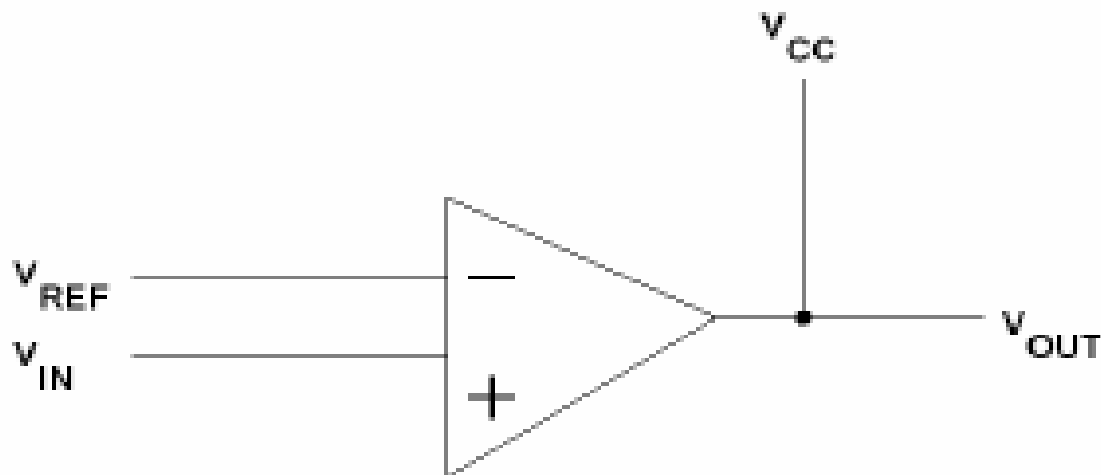




Dept. of Computer Science and Engineering
University of Rajshahi
www.ru.ac.bd

Dr. Shamim Ahmad

Flash (Parallel) Converter




If $V_{IN} > V_{REF}$ then $V_{OUT} = V_{CC}$ (Logic high)

If $V_{IN} < V_{REF}$ then $V_{OUT} = 0$ (Logic low)

An n-bit flash converter uses $2^n - 1$ comparators

Flash (Parallel) Converter

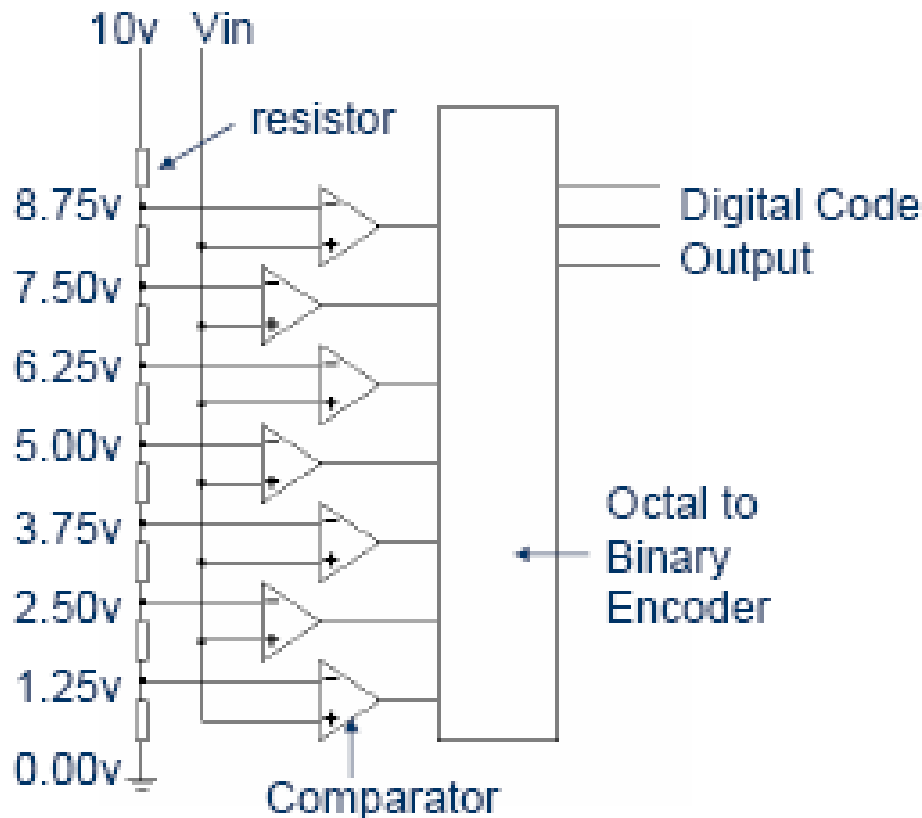

Example-



If $V_{in} = 6.00v$, then the first 4 comparators from the bottom will return a logic high signal while the top three will return a low signal.

Octal 4 = Binary 100

Flash (Parallel) Converter

- **Advantages**
 - Very Fast
- **Disadvantages**
 - Lower resolution (many comparators are required for higher resolution: 8 bit = 255 comparators)
 - Higher cost

Dual-Slope Converter

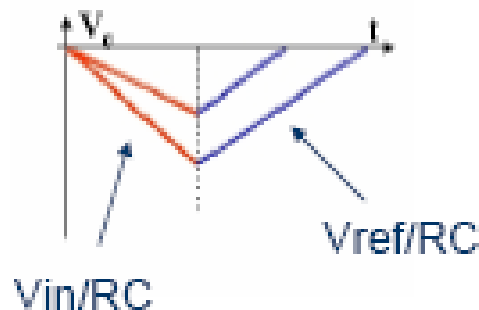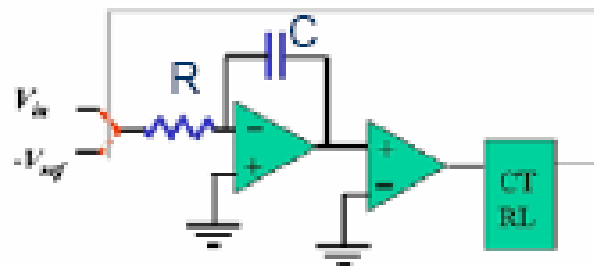

CTRL allows capacitor (C) to charge with rate given by V_{in}/RC for time T_0 (N_0 clock cycles). Then CTRL switched and allows capacitor to discharge for to time T_1 (N_1 clock cycles) at a rate given by V_{ref}/RC .

$$V_{ref}/N_1 = V_{in}/N_0$$


V_{ref} and N_0 are known and N_1 is measured, so:

$$V_{in} = (N_1/N_0)V_{ref}$$

Dual-Slope Converter

- **Advantages**
 - Higher resolution
 - Higher accuracy
 - Lower cost
 - Good noise immunity
- **Disadvantages**
 - Slow

Voltage-to-Frequency Converters

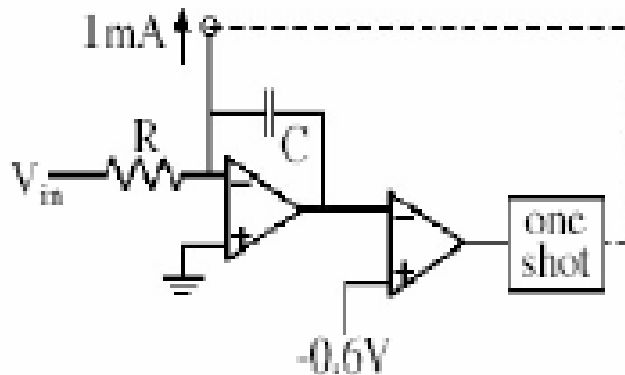


Converter takes in a voltage (V_{in}) and returns a series of pulses. Frequency of pulses is proportional to V_{in} .

Voltage-to-Frequency Converters

- Advantages
 - Excellent noise reduction
- Disadvantages
 - Slow
 - Generally limited to 10bits or less

Successive Approximation Converter

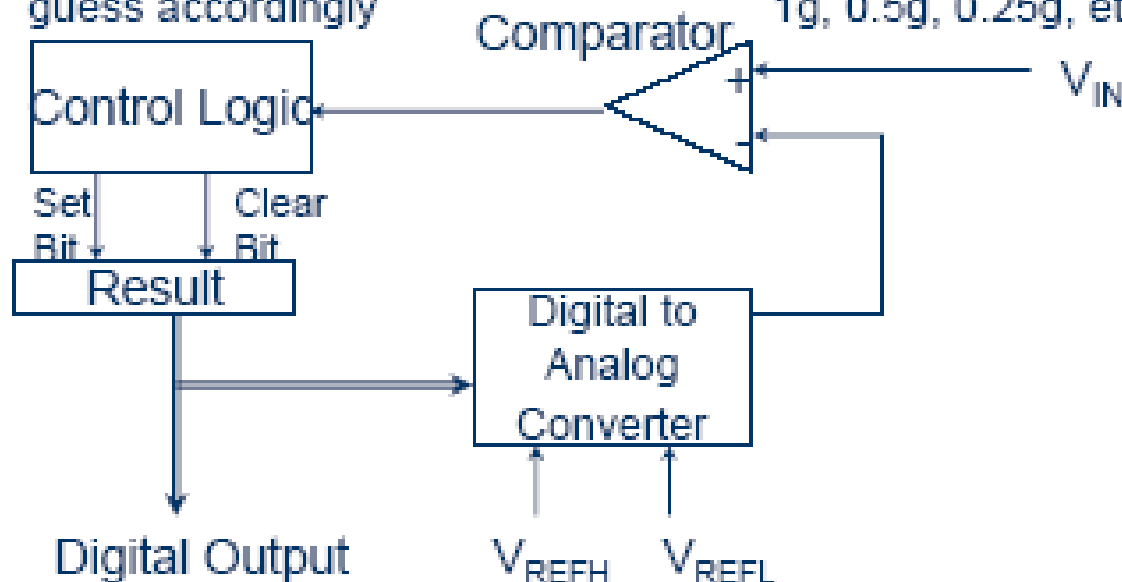- Guess the answer, use a D/A to convert it to an analog voltage and compare it to the voltage being measured – adjust your guess accordingly
- Similar to the ordering weighing (on a scale) of an unknown quantity on a precision balance, using a set of weights, such as 1g, 0.5g, 0.25g, etc.



Successive Approximation Converter

- Reliable
- Capable of high speed
- Conversion time is clock rate times number of bits.
 - Example with 8-bit, 2-MHz clock rate:
 - Conversion time= (clock period) x (#bits being converted)
 - Conversion time= (0.5 micro-sec) x (8-bits) = 4 μ s

Successive Approximation Example

- 10-bit resolution or $0.0009765625V$ of V_{ref}
- $V_{in} = 0.6V$
- $V_{ref} = 1V$
- Find the digital value of V_{in}

Bit	Voltage
1	.5
2	.25
3	.125
4	.0625
5	.03125
6	.015625
7	.0078125
8	.00390625
9	.001952125
10	.0009765625

Successive Approximation Example (cont.)

- Calculate the state of MSB-1 (bit 2)
 - Compare $V_{in} = 0.6V$ and $V = V_{ref}/2 + V_{ref}/4 = 0.5 + 0.25 = 0.75V$
 - Since $0.6 < 0.75 \rightarrow$ MSB-1 = 0 (turned off)
- Calculate the state of MSB-2 (bit 3)
 - Go back to the last voltage value that caused it to be turned on (in this case 0.5V) and add $V_{ref}/8$ to it and compare with V_{in} .
 - Compare V_{in} and $(0.5 + (V_{ref}/8)) = 0.625$
 - Since $0.6 < 0.625 \rightarrow$ MSB-2 = 0 (turned off)

1	0	0							
---	---	---	--	--	--	--	--	--	--

Successive Approximation Example (cont.)

- Calculate the state of MSB-3 (bit 4)
 - Go back to the last voltage value that caused it to be turned on (in this case 0.5V) and add $V_{\text{ref}}/16$ to it and compare with V_{in} .
 - Compare V_{in} and $(0.5 + (V_{\text{ref}}/16))=0.5625$
 - Since $0.6 > 0.5625 \rightarrow \text{MSB-3} = 1$ (turned on)


MSB	MSB-1	MSB-2	MSB-3	...					
1	0	0	1						

Successive Approximation Example (cont.)

- Digital Results:

MSB	MSB-1	MSB-2	MSB-3	...					LSB
1	0	0	1	1	0	0	1	1	0

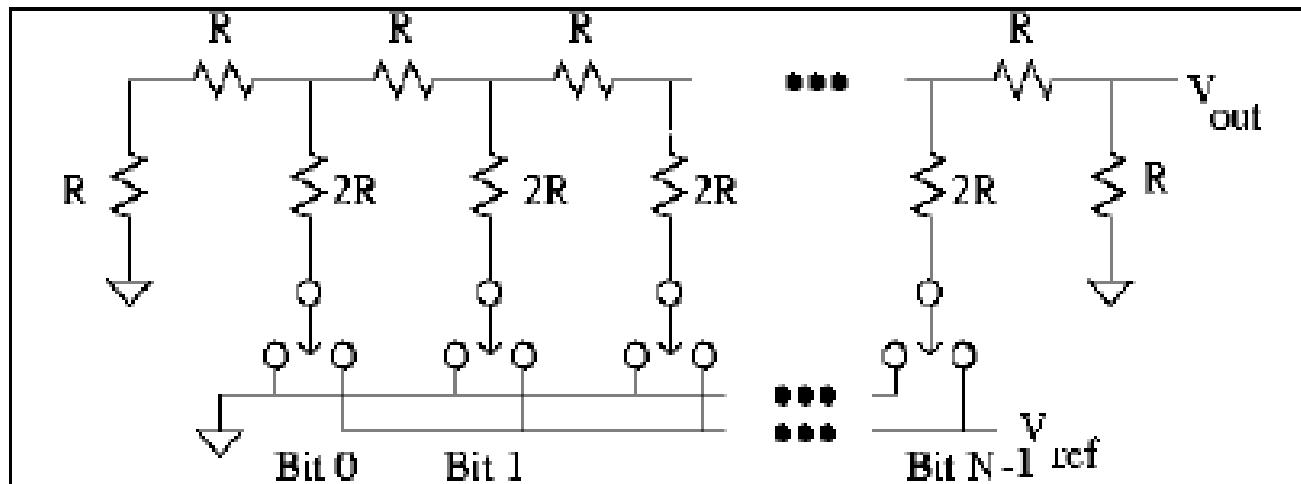
- Results = $\frac{1}{2} + \frac{1}{16} + \frac{1}{32} + \frac{1}{256} + \frac{1}{512} = .599609375 \text{ V}$




$$V_{out} = \frac{1}{6} V_{ref} \left[B_7 + \frac{1}{2} B_6 + \frac{1}{4} B_5 + \dots + \frac{1}{128} B_0 \right]$$

- Note that the driving point impedance (resistance) is the same for each cell.
- R-2R Ladder achieves large current division ratios with only two resistor values

Successive-Approximation A/D

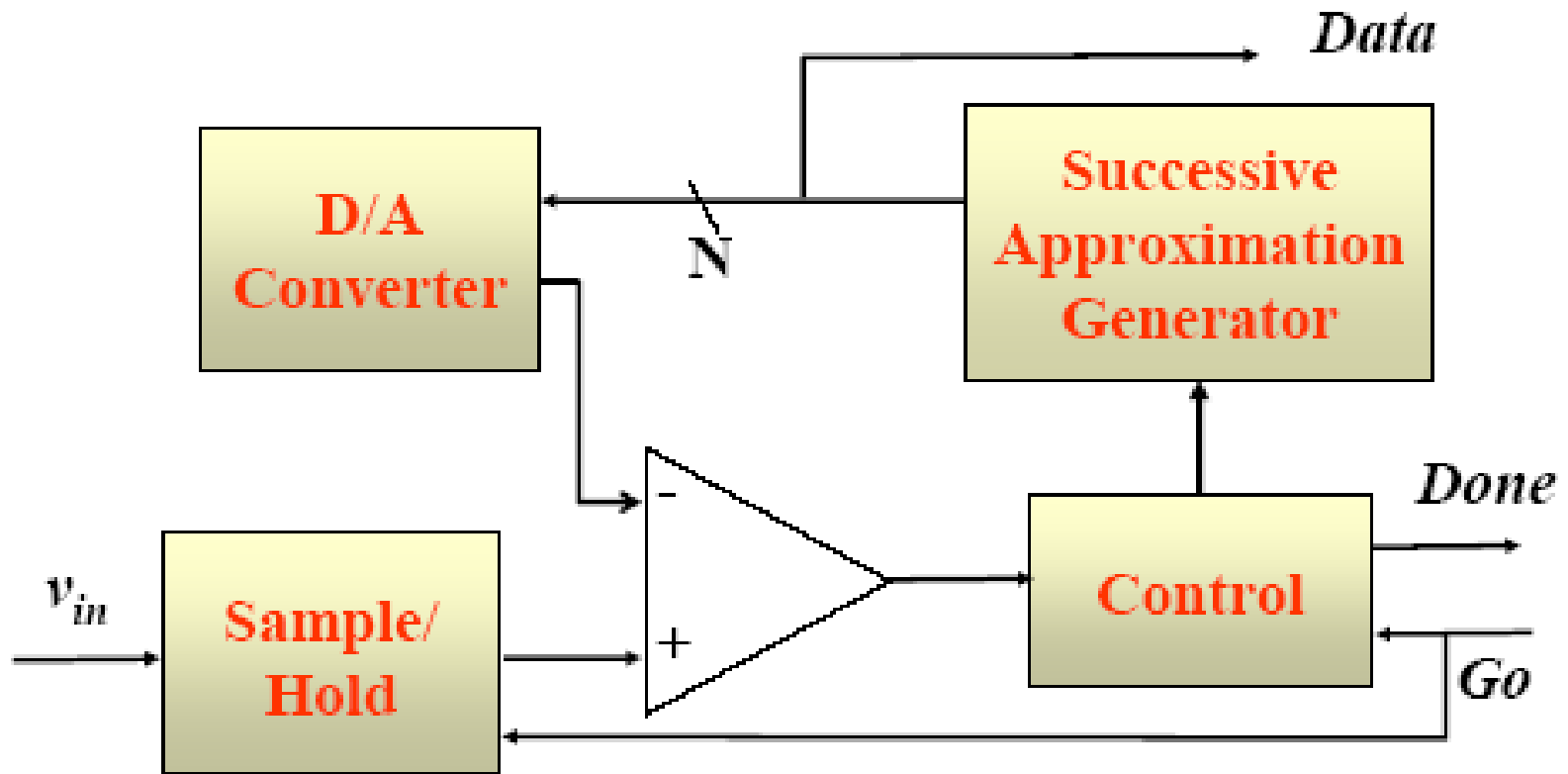

Flash A/D Converter

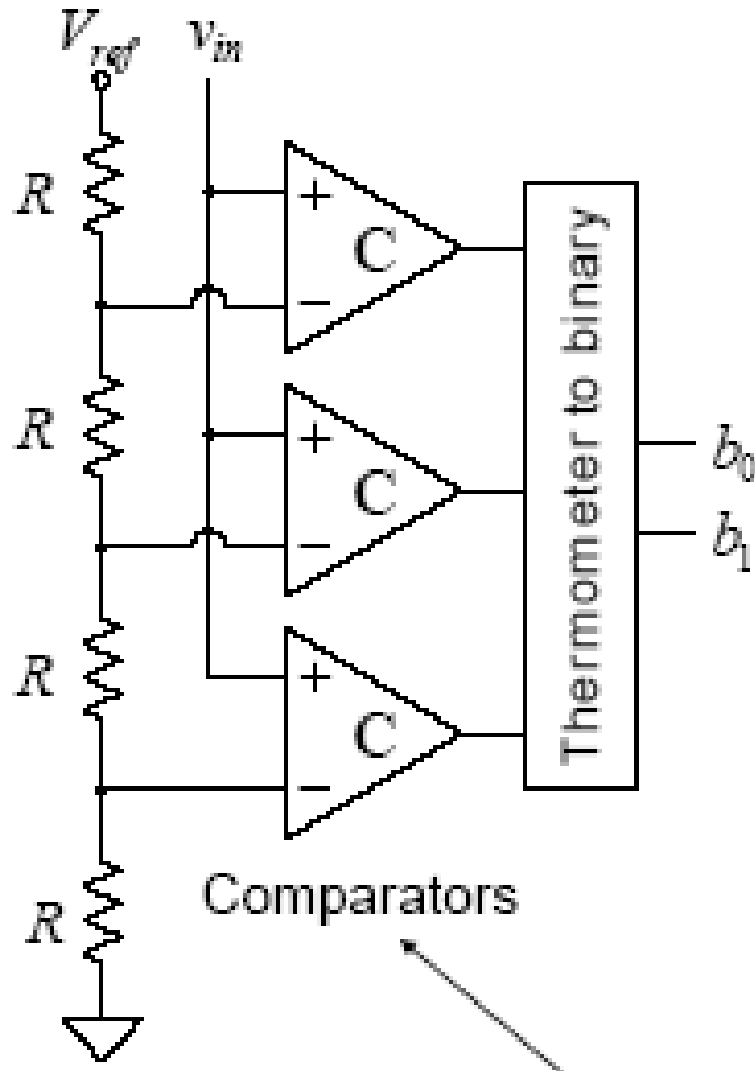

Brute-force
conversion

A/D

Simultaneously compare
the
analog value with every
possible reference value

Fastest method of A/D
conversion


ize scales exponentially
with precision

(requires
comparators)


2N

ADC 0809

Block Diagram

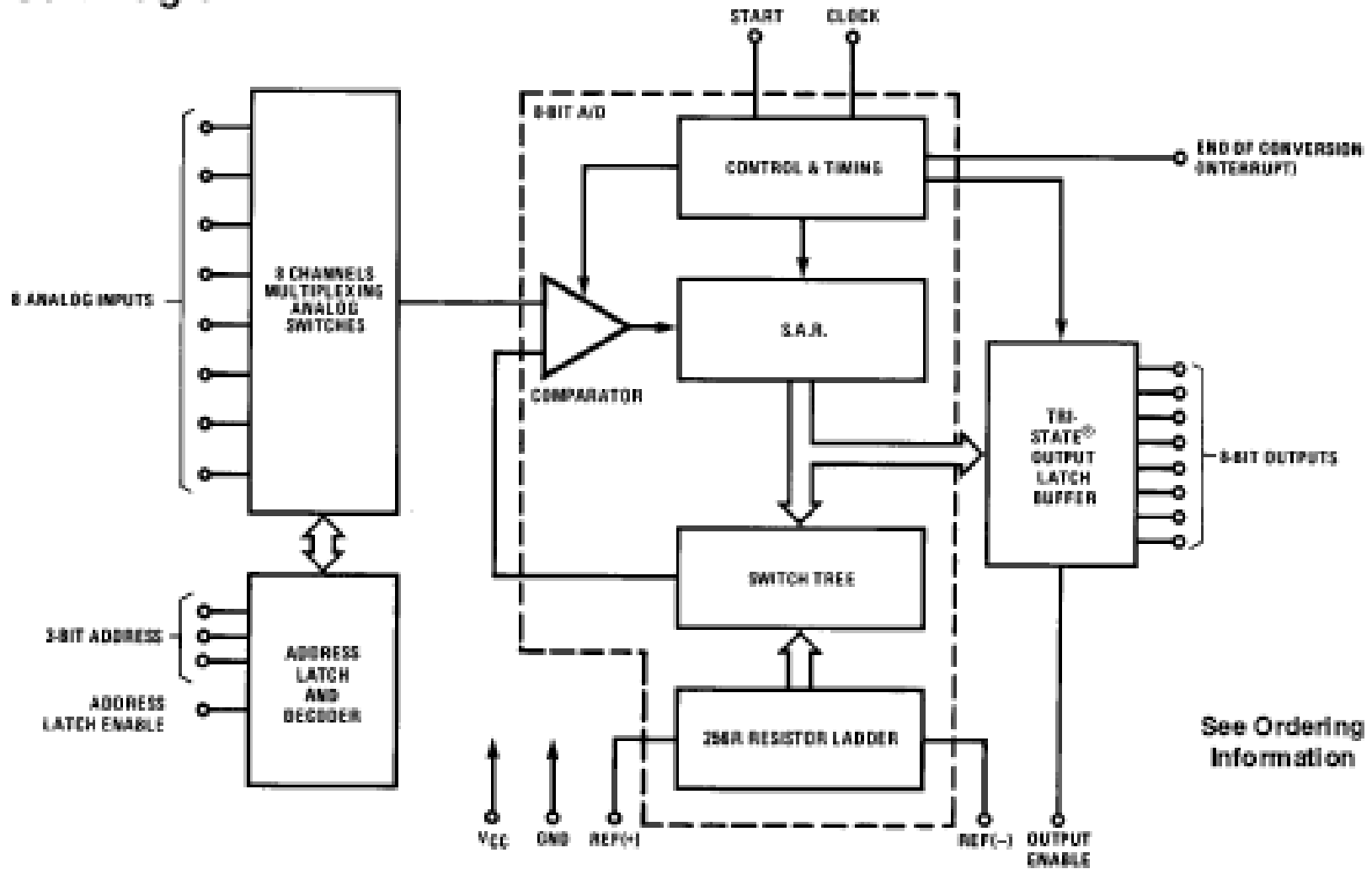


Dual-In-Line Package

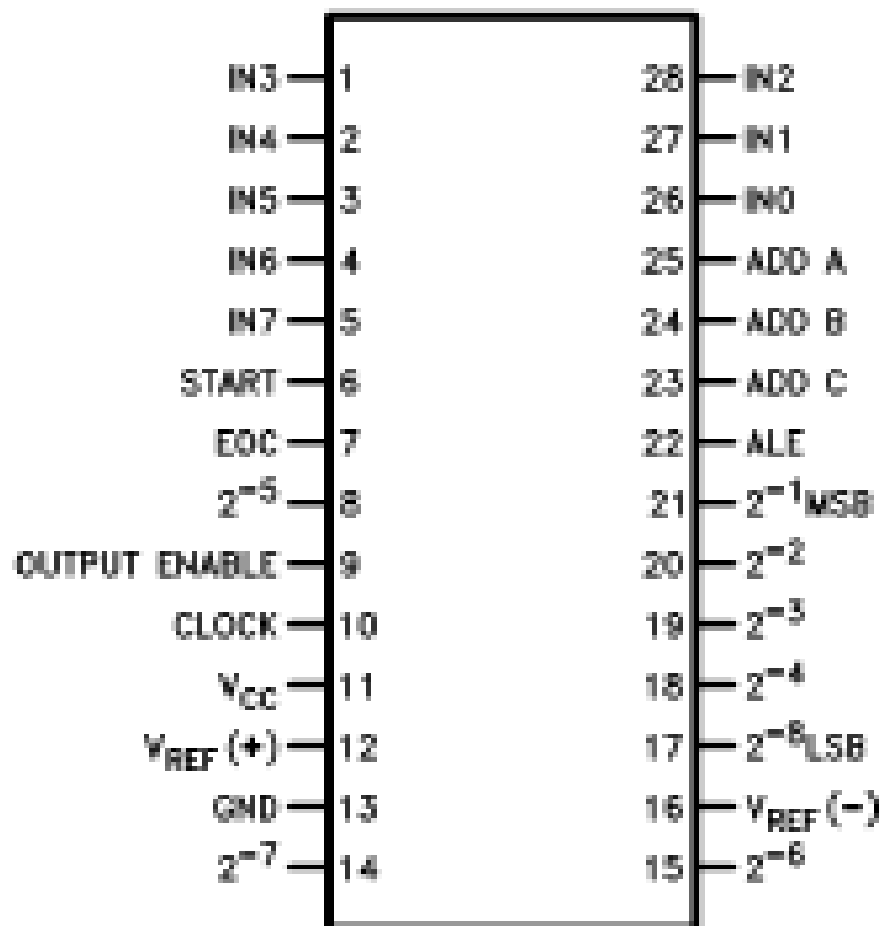


TL/H/9872-11

Order Number ADC0808CCN, ADC0809CCN,
ADC0808CCJ or ADC0809CJ
See NS Package J28A or N28A

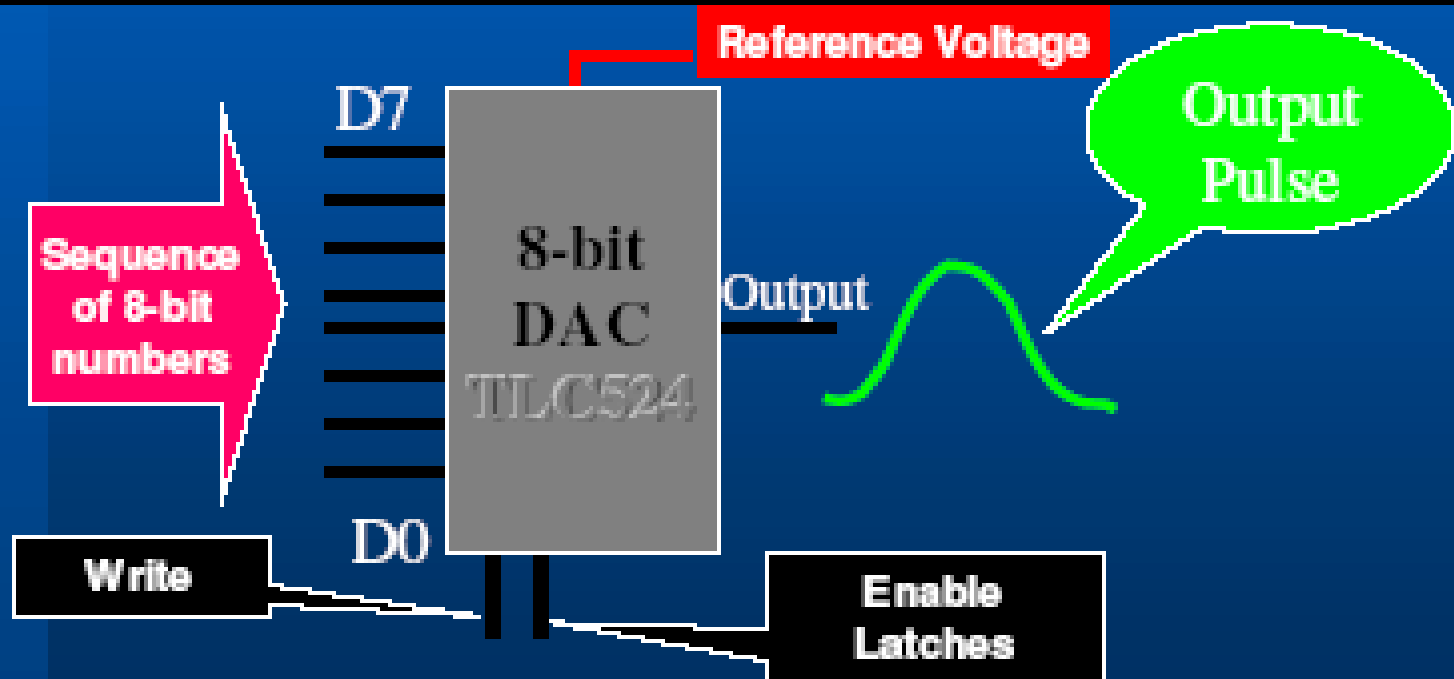The **DIGITAL to ANALOG CONVERTERS (DAC)** are devices that convert digital to analog signals:




Summing Amplifier

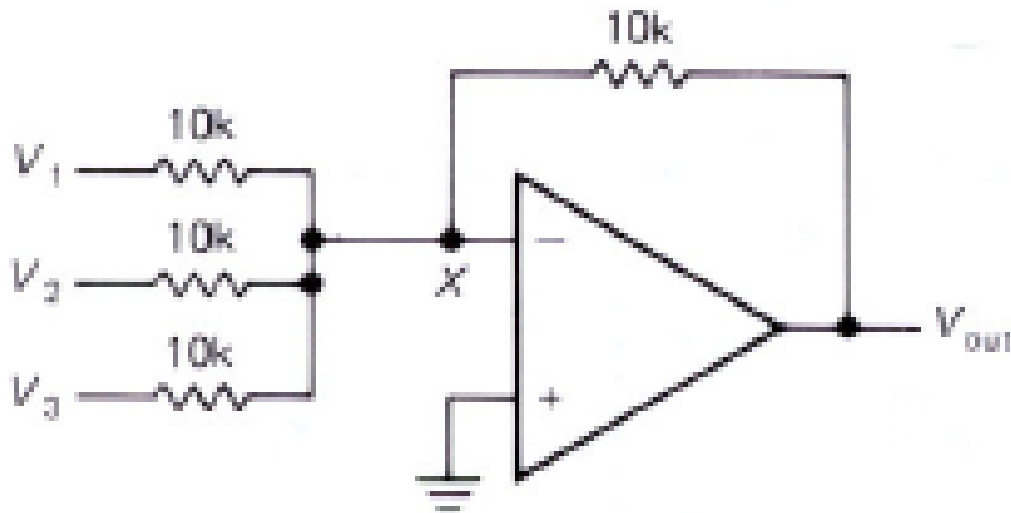

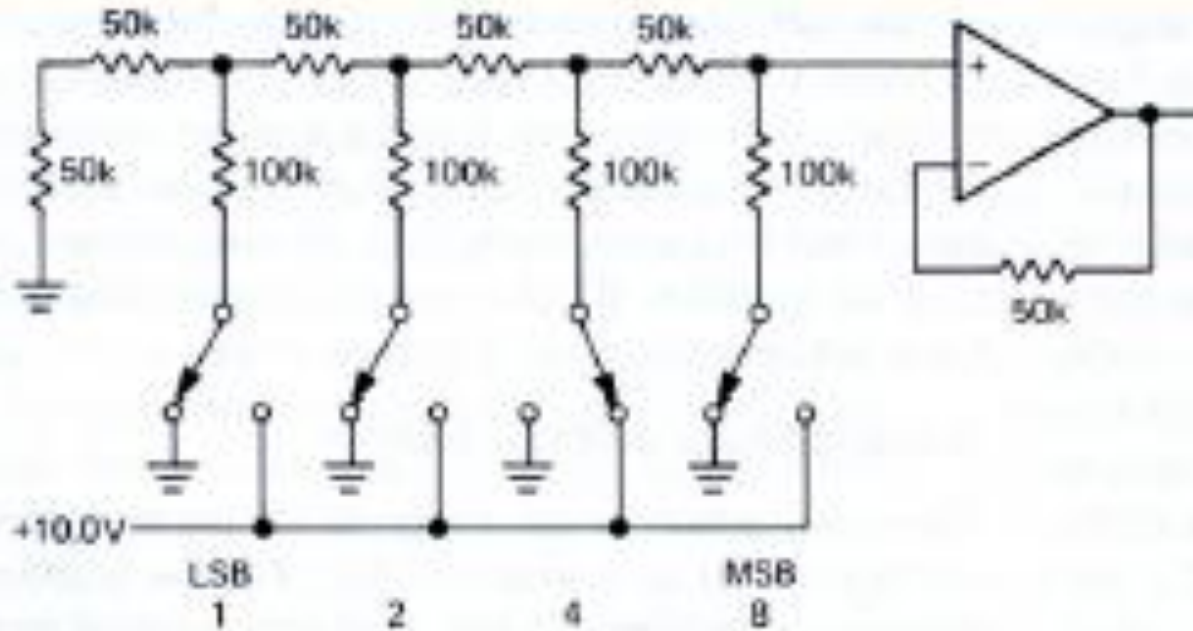
Exercise : Show that $V_{out} = - (V_1 + V_2 + V_3)$

R-2R Network to convert Digital to Analog



**By now you should know how does
It work...**

Output Op-Amp

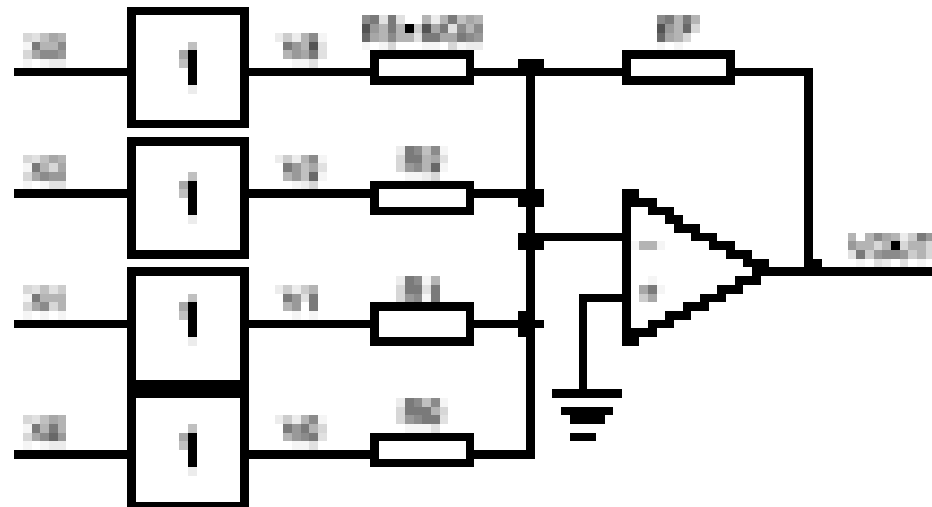

$$V_{OUT} = \frac{-R_1}{R_{SUM}} \times V_{SUM} = -R_1 (V_1 G_1 + V_2 G_2 + V_3 G_3 + V_4 G_4)$$