

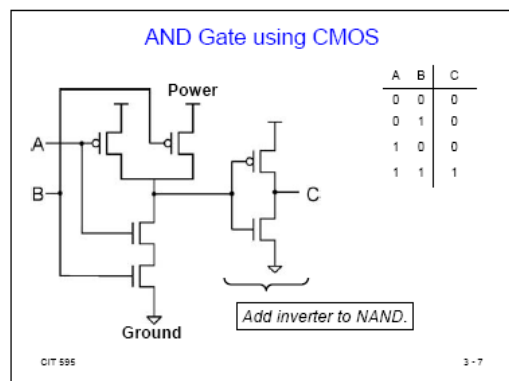


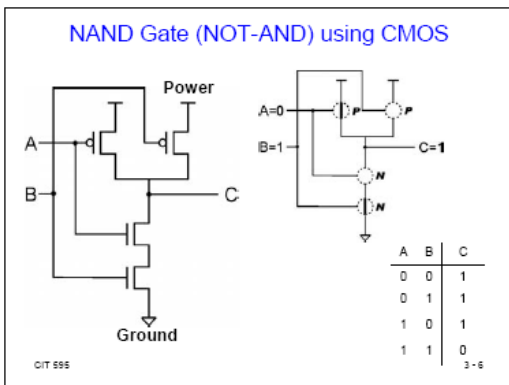


Dept. of Computer Science and Engineering
 University of Rajshahi
 www.ru.ac.bd


Dr. Shamim Ahmad

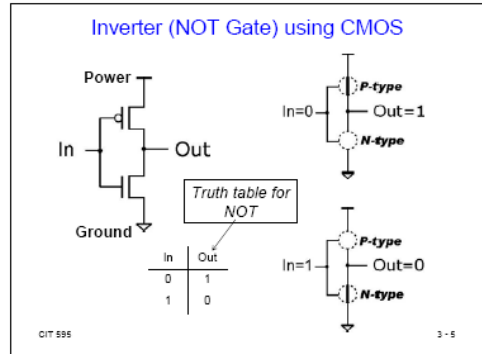

■ Combinational and Sequential Circuits

 

 ■ Block Diagram of Combinational Circuits




■ Analysis Procedure of a Combinational Circuit

1. Make sure the given circuit is a combinational circuit
 - Combinational Circuit without feedback paths or memory elements
 - Feedback paths in digital circuits define a sequential circuit
2. Obtain the output Boolean functions or the truth table

■ Procedure to Obtain the Output Boolean Functions from a Logic Diagram

1. Label all gate outputs that are a function of input variables with arbitrary symbol. Determine the Boolean functions for each gate output.
2. Label the gates that are a function of input variables and previously labeled gates with other arbitrary symbols. Find the Boolean functions for these gates.
3. Repeat the process outline in step 2 until the outputs of the circuits are obtained
4. By repeated substitution of previously defined functions, obtain the output Boolean function in terms of input variables.

■ Procedure Example

 

■ Procedure Example

Step 1:

$$F_2 = AB + AC + BC$$

$$T_1 = A + B + C$$

$$T_2 = ABC$$

Step 2:

$$T_3 = F_2' T_1$$

$$F_1 = T_3 + T_2$$

Step 3-4:

$$F_1 = T_3 + T_2 = F_2' T_1 + ABC$$

$$= (AB + AC + BC)' (A + B + C) + ABC$$

$$= A'BC' + A'B'C + AB'C' + ABC$$

■ Procedure to Obtain the Output Boolean Functions from the Truth Table

1. Determine the number of input variables in the circuit. For n inputs, form the 2^n possible input combinations and list the binary numbers from 0 to $2^n - 1$ in a table
2. Label the output of the selected gates with arbitrary symbols
3. Obtain the truth table for the outputs of those gates that are a function of the input variables only
4. Proceed to obtain the truth table for the outputs of those gates that are a function of previously defined values until the columns for all outputs are determined

■ Procedure Example

			Procedure →					
A	B	C	F_2	F_2'	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

Truth Table for Example

Boolean Operator

- A Boolean operator can be completely described using a truth table
- The truth table for the Boolean operators AND and OR are shown at the right
- The AND operator is also known as a "Boolean product". It is also represented with dot symbol. E.g. $x \cdot y$
- The OR operator is the "Boolean sum". It is also represented with "+" symbol. E.g. $x + y$
- The NOT operation is most often designated by an overbar. It is sometimes indicated by a prime mark (') or an "elbow" (~) or tilda (~)

X AND Y		
X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1

X OR Y		
X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT X	
X	\bar{X}
0	1
1	0

CIT 595

3 - 12

Boolean Operator Precedence

- As with common arithmetic, Boolean operations have rules of precedence
- The NOT operator has highest priority, followed by AND and then OR
- Hence to evaluate the expression, z is negated first, then x is ANDed with the previous result and finally ORed with y

$F(x, y, z) = x\bar{z} + y$					
x	y	z	\bar{z}	$x\bar{z}$	$x\bar{z} + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

CIT 595

3 - 14

Boolean Identity Group I

- Most Boolean identities have an AND (product) form as well as an OR (sum) form. We give our identities using both forms. Our first group is rather intuitive:

Identity Name	AND Form	OR Form
Identity Law	$1x = x$	$0 + x = x$
Null Law	$0x = 0$	$1 + x = 1$
Idempotent Law	$xx = x$	$x + x = x$
Inverse Law	$x\bar{x} = 0$	$x + \bar{x} = 1$

CIT 595

3 - 16

Boolean Identity Group II

- Our second group of Boolean identities should be familiar to you from your study of algebra:

Identity Name	AND Form	OR Form
Commutative Law	$xy = yx$	$x+y = y+x$
Associative Law	$(xy)z = x(yz)$	$(x+y)+z = x+(y+z)$
Distributive Law	$x+yz = (x+y)(x+z)$	$x(y+z) = xy+xz$

CIT 595

3 - 17

Boolean Identity Group III

- Our last group of Boolean identities are perhaps the most useful.
- If you have studied set theory or formal logic, these laws are also familiar to you.

Identity Name	AND Form	OR Form
Absorption Law	$x(x+y) = x$	$x + xy = x$
DeMorgan's Law	$\overline{(xy)} = \bar{x} + \bar{y}$	$\overline{(x+y)} = \bar{x}\bar{y}$
Double Complement Law	$\overline{(\bar{x})} = x$	

CIT 595

3 - 18

Example using Boolean Identity

- We can use Boolean identities to simplify the function:

$$\begin{aligned}
 &(x + y)(x' + y) \\
 &= xx' + xy + yx' + yy \quad \text{Distributive Law} \\
 &= 0 + xy + yx' + y \quad \text{Inverse \& Idempotent Law} \\
 &= xy + yx' + y \quad \text{Identity Law} \\
 &= y(x + x') + y \quad \text{Distributive Law} \\
 &= y(1) + y \quad \text{Inverse Law} \\
 &= y + y \quad \text{Identity Law} \\
 &= y \quad \text{Idempotent Law}
 \end{aligned}$$

CIT 595

3 - 19

De Morgan's Law

- Sometimes it is more economical to build a circuit using the complement of a function (and complementing its result) than it is to implement the function directly
- DeMorgan's law provides an easy way of finding the complement of a Boolean function

$$\overline{(xy)} = \bar{x} + \bar{y} \quad \text{and} \quad \overline{(x+y)} = \bar{x}\bar{y}$$

CIT 595

3 - 20

Standard or Canonical Form

- There are two canonical forms for Boolean expressions: *sum-of-products* and *product-of-sums*
 - Recall the Boolean product is the AND operation and the Boolean sum is the OR operation.
- In the sum-of-products form, ANDed variables are ORed together.
 - For example: $F(x, y, z) = xy + xz + yz$
- In the product-of-sums form, ORed variables are ANDed together.
 - For example: $F(x, y, z) = (x+y)(x+z)(y+z)$

CIT 595

3 - 23

Conversion to Sum-of-Products Form

- It is easy to convert a function to sum-of-products form using its truth table
- We are interested in the values of the variables that make the function "true" (i.e. output 1)
- Using the truth table, we list the values of the variables that result in a true value
 - The variables corresponding to row with output 1 are "ANDed"
 - If the variable's input value is 1 then it is written as it is else the complement of that variable is written
- Each group of variables is then "Ored" together

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

CIT 595

3 - 24

Conversion to Sum-of-Products form (contd..)

- The sum-of-products form for function is:

$$F(x, y, z) = \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}\bar{z} + xy\bar{z} + xyz$$

One ANDed Group is known as Minterm

Note: This function is not in simplest terms. It was just show how the function can be rewritten in canonical sum-of-products form.

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

CIT 595

3 - 25

Conversion to Product-of-Sums

- We are interested in the values of the variables that make the function "false" (i.e. output 0)
- Using the truth table, we list the values of the variables that result in a false value
 - The variables corresponding to row with output 0 are "ORed"
 - If the variable's input value is 0 then it is written as it is else the complement of that variable is written
- Each group of variables is then "ANDed" together

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

CIT 595

3 - 26

Conversion to Product-of-Sums (contd..)

- The sum-of-products form for function is:

$$(x + y + z)(x + y + \bar{z})(\bar{x} + y + \bar{z})$$

One ORed Group is known as Maxterm

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

CIT 595

3 - 27

Logic Gate


- We have looked at Boolean functions in abstract terms
- In this section, we see that Boolean functions are implemented in digital computer circuits are called gates
- A gate is an electronic device that produces a result based on one or more input values
 - In reality, gates consist of one to six transistors, but digital designers think of them as a single unit
 - Integrated circuits contain collections of gates suited to a particular purpose

CIT 555

3 - 28

Basic Gates

 - The three simplest gates are the AND, OR, and NOT gates




- They correspond directly to their respective Boolean operations, as you can see by their truth tables

CIT 555

3 - 29

XOR Gate

- Another very useful gate is the exclusive OR (XOR) gate
- The output of the XOR operation is true only when the values of the inputs differ

 

CIT 555

3 - 30


4 Possible Operations for Addition of Two Binary Digits

$$\begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0
 \end{array}
 \qquad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 1
 \end{array}$$


$$\begin{array}{r}
 1 \\
 + 0 \\
 \hline
 1
 \end{array}
 \qquad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 10
 \end{array}$$

1 0
↑
Carry

■ Half Adder

 

■ Half Adder

 


■ Full Adder

1. Full adders perform the arithmetic sum of three bits
2. Full adders is implemented by a 3-input 2-output combinational circuit
3. Truth Table:

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Binary Multiplier

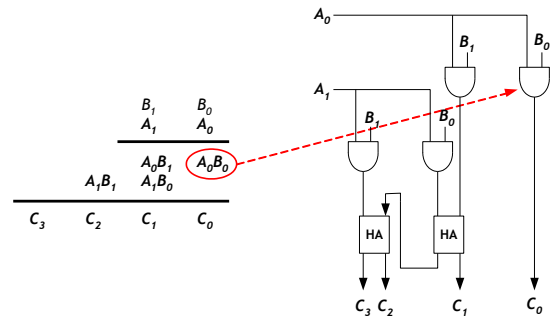

Universal Gates

- NAND and NOR are known as *universal gates* because they are inexpensive to manufacture and any Boolean function can be constructed using only NAND or only NOR gates

NOT X

X AND Y

X OR Y

CIT 595 3 - 32

NAND and NOR gates

- NAND and NOR are two very important gates. Their symbols and truth tables are shown at the right

X NAND Y

X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0

X NOR Y

X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

CIT 595 3 - 31

Kmap for Sum-Of-Product Form

- The output values placed in each cell of the matrix are derived from the "minterms" of a Boolean function
- A *minterm* is a **product** term that contains all of the function's variables exactly once, either complemented or not complemented

CIT 595 3 - 38

Minterm Example with Two variables

- For example, the minterms for a function having the inputs x and y are: $\bar{x}\bar{y}$, $\bar{x}y$, $x\bar{y}$, and xy

Minterm	X	Y
$\bar{x}\bar{y}$	0	0
$\bar{x}y$	0	1
$x\bar{y}$	1	0
xy	1	1

Note: If variable input is 1, then it is written as it is else the complement of that variable is written

CIT 595 3 - 39

Minterm Example with Three variables

- Similarly, a function having three inputs, has the minterms that are shown in this diagram

Minterm	X	Y	Z
$\bar{x}\bar{y}\bar{z}$	0	0	0
$\bar{x}\bar{y}z$	0	0	1
$\bar{x}y\bar{z}$	0	1	0
$\bar{x}yz$	0	1	1
$x\bar{y}\bar{z}$	1	0	0
$x\bar{y}z$	1	0	1
$xy\bar{z}$	1	1	0
xyz	1	1	1

CIT 595

3 - 40

Kmap Cell using SOP form: Example 1

- A Kmap has a cell for each minterm
- This means that it has a cell for each line for the truth table of a function
- The truth table for the function $F(x,y) = xy$ is shown at the right along with its corresponding Kmap

$F(x,y) = xy$		
X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1

X \ Y	0	1
0	0	0
1	0	1

CIT 595

3 - 41

Kmap Cell using SOP Form: Example 2

- As another example, we give the truth table and Kmap for the function, $F(x,y) = x + y$
- This function is equivalent to the OR of all of the minterms that have a value of 1 (Sum of Product Form). Thus:

$$F(x,y) = X+Y = \bar{x}y + x\bar{y} + xy$$

$F(x,y) = x+y$		
X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1

X \ Y	0	1
0	0	1
1	1	1

CIT 595

3 - 42

Kmap Simplification for Two Variables using SOP Form

- Of course, the minterm function that we derived from our Kmap was not in simplest terms
 - That's what we started with in this example
- We can, however, reduce our complicated expression to its simplest terms by finding adjacent 1s in the Kmap that can be collected into groups that are "powers of two"
- In our example, we have two such groups
 - Can you find them?

X \ Y	0	1
0	0	1
1	1	1

CIT 595

Example 2

3 - 43

Reduced Expression for Example 2

- In the "green" group (vertical), it does not matter what value x has, hence the group is only dependent on variable y
- Similarly in the "pink" group (horizontal), it does not matter what value y has, the group is only dependent on variable x
- Hence the Boolean function reduces to $x + y$

x \ y	0	1
0	0	1
1	1	1

CIT 595

3 - 44

Kmap Simplification for Two Variables using SOP Form

- The best way of selecting two groups of 1s from our simple Kmap is shown below
- We see that both groups are powers of two and that the groups overlap.
- The next slide gives guidance for selecting Kmap groups

x \ y	0	1
0	0	1
1	1	1

CIT 595

3 - 45

Rules for Kmap Simplification using Sum of Products Form (SOP)

The rules of Kmap simplification are:

- Groupings can contain only 1s; no 0s
- Groups can be formed only at right angles; diagonal groups are not allowed
- The number of 1s in a group must be a power of 2 – even if it contains a single 1
- The groups must be made as large as possible
- Groups can overlap and wrap around the sides of the Kmap

CIT 595

3 - 46

Kmap with Three Variables (SOP form)

- A Kmap for three variables is constructed as shown in the diagram below
- We have placed each minterm in the cell that will hold its value
 - Notice that the values for the yz combination at the top of the matrix form a pattern that is not a normal binary sequence
- A Kmap must be ordered so that each minterm differs only in one variable from each neighboring cell hence 11 appears before 10 – Rule!! (will help simplification)

x \ yz	00	01	11	10
0	$\bar{x}\bar{y}\bar{z}$	$\bar{x}y\bar{z}$	$x\bar{y}\bar{z}$	$x\bar{y}z$
1	$x\bar{y}\bar{z}$	$x\bar{y}z$	$xy\bar{z}$	xyz

CIT 595

3 - 47

Kmap with Three Variables (SOP Form)

Note:

- Thus, the first row of the Kmap contains all minterms where x has a value of zero
- The first column contains all minterms where y and z both have a value of zero

X \ YZ	00	01	11	10
0	$\bar{x}\bar{y}\bar{z}$	$\bar{x}\bar{y}z$	$\bar{x}yz$	$\bar{x}y\bar{z}$
1	$x\bar{y}\bar{z}$	$x\bar{y}z$	xyz	$xy\bar{z}$

CIT 595

3 - 48

Kmap - Three Variable (SOP Form): Example 1

- Consider the function:

$$F(X, Y, Z) = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}\bar{z} + xyz$$

- Its Kmap is given below:

- What is the largest group of 1s that is a power of 2?

X \ YZ	00	01	11	10
0	0	1	1	0
1	0	1	1	0

CIT 595

3 - 49

Kmap - Three Variable (SOP form): Example 1

- This grouping tells us that changes in the variables x and y have no influence upon the value of the function: They are irrelevant
- This means that the function,

$$F(X, Y, Z) = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}\bar{z} + xyz$$

reduces to $F(X, Y, Z) = Z$

You could verify this reduction with identities or a truth table.

X \ YZ	00	01	11	10
0	0	1	1	0
1	0	1	1	0

CIT 595

3 - 50

Kmap - Three Variable (SOP Form): Example 2

- Now for a more complicated Kmap. Consider the function:

$$F(X, Y, Z) = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}yz + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$$

- Its Kmap is shown below. There are (only) two groupings of 1s.

- Can you find them?

X \ YZ	00	01	11	10
0	1	1	1	1
1	1	0	0	1

CIT 595

3 - 51

Kmap - Three Variable (SOP form): Example 2

- In this Kmap, we see an example of a "group that wraps around the sides" of a Kmap.
- This group tells us that the values of x and y are not relevant to the term of the function that is encompassed by the group
 - What does this tell us about this term of the function?
 - It is dependent on \bar{z}

What about the green group in the top row?

X \ YZ	00	01	11	10
0	1	1	1	1
1	1	0	0	1

CIT 595

3 - 52

Kmap - Three Variable (SOP): Example 2

- The "green group" in the top row tells us that only the value of x is significant in that group.
- We see input value of x is 0 i.e. minterm is complemented in that row, so the other term of the reduced function is \bar{x}
- Our reduced function is: $F(x,y,z) = \bar{x} + \bar{z}$

Recall that we had six minterms in our original function !!
The function is considerably minimized

X \ YZ	00	01	11	10
0	1	1	1	1
1	1	0	0	1

CIT 595

3 - 53

Kmap Simplification for Four Variables (SOP Form)

- The model can be extended to accommodate the 16 minterms that are produced by a four-input function
- This is the format for a 16-minterm Kmap

WX \ YZ	00	01	11	10
00	$\bar{w}\bar{x}\bar{y}\bar{z}$	$\bar{w}\bar{x}\bar{y}z$	$\bar{w}\bar{x}y\bar{z}$	$\bar{w}\bar{x}yz$
01	$\bar{w}x\bar{y}\bar{z}$	$\bar{w}x\bar{y}z$	$\bar{w}xy\bar{z}$	$\bar{w}xyz$
11	$wx\bar{y}\bar{z}$	$wx\bar{y}z$	$wxy\bar{z}$	$wxyz$
10	$wx\bar{y}\bar{z}$	$wx\bar{y}z$	$wxy\bar{z}$	$wxyz$

CIT 595

3 - 54

Kmap Four Variables (SOP Form) Example

- We have populated the Kmap shown below with the nonzero minterms from the function:

$$F(W, X, Y, Z) = \bar{w}\bar{x}\bar{y}\bar{z} + \bar{w}\bar{x}\bar{y}z + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}yz + \bar{w}x\bar{y}\bar{z} + \bar{w}x\bar{y}z + \bar{w}xy\bar{z} + \bar{w}xyz$$

Can you identify (only) three groups in this Kmap?

Recall the Rules of Simplification

WX \ YZ	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

CIT 595

3 - 55

Kmap Four Variables (SOP Form) Example

- The three groups consist of:
 - A purple group entirely within the Kmap at the right
 - A pink group that wraps the top and bottom
 - A green group that spans the corners
- Thus we have three terms in our final function:

$$F(W, X, Y, Z) = \bar{X}Y + \bar{X}Z + WYZ$$

YZ	00	01	11	10
WX 00	1	1		1
01	1		1	1
11				
10	1	1		1

CIT 595

3 - 56

Choosing Kmap Groups

- It is possible to have a choice as to how to pick groups within a Kmap, while keeping the groups as large as possible
- The (different) functions that result from the groupings below are logically equivalent

YZ	00	01	11	10
WX 00	1		1	
01	1		1	1
11	1			
10	1			

YZ	00	01	11	10
WX 00	1		1	
01	1		1	1
11	1			
10	1			

CIT 595

3 - 57

Don't Care Conditions

- Real circuits don't always need to have an output defined for every possible input
 - For example, some calculator displays consist of 7-segment LEDs. These LEDs can display $2^7 - 1$ patterns, but only ten of them are useful
- If a circuit is designed so that a particular set of inputs can never happen, we call this set of inputs a *don't care* condition
- They are very helpful to us in Kmap circuit simplification



CIT 595

3 - 58

Don't Care Example (SOP Form)

- In a Kmap, a don't care condition is identified by an X in the cell of the minterm(s) for the don't care inputs, as shown below
- In performing the simplification, we are free to include or ignore the X's when creating our groups

YZ	00	01	11	10
WX 00	X	1	1	X
01		X	1	
11	X		1	
10			1	

CIT 595

3 - 59

Don't Care Example (SOP Form)

- In one grouping in the Kmap below, we have the function:

$$F(W, X, Y, Z) = \bar{W}\bar{X} + YZ$$

YZ \ WX	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

CIT 555

3-60

Don't Care Example w/ Different Grouping

- A different grouping gives us the function:

$$F(W, X, Y, Z) = \bar{W}Z + YZ$$

YZ \ WX	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

CIT 555

3-61

Don't Care Condition Example

- The truth table of: $F(W, X, Y, Z) = \bar{W}Z + YZ$ is different from the truth table of:

$$F(W, X, Y, Z) = \bar{W}\bar{X} + YZ$$

- However, the values for which they differ, are the inputs for which we have don't care conditions

YZ \ WX	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

CIT 555

3-62

Kmap using Product-of-Sum (POS) Form

- The output values placed in each cell are derived from the "maxterm" of a Boolean function
- A *maxterm* is a sum term that contains all of the function's variables exactly once, either complemented or not complemented

CIT 555

3-64

Maxterm Example

X	Y	Maxterm
0	0	$X + Y$
0	1	$X + Y'$
1	0	$X' + Y$
1	1	$X' + Y'$

Note: If variable input is 0, then it is written as it is else the complement of that variable is written

CIT 595

3 - 66

Kmap Rules using Product-of-Sum Form

- Groupings can contain only 0s; no 1s
- Groups can be formed only at right angles; diagonal groups are not allowed
- The number of 0s in a group must be a power of 2 – even if it contains a single 0
- The groups must be made as large as possible
- Groups can overlap and wrap around the sides of the Kmap
- Use don't care conditions when you can

CIT 595

3 - 66

Binary Adder-Subtractor


■ Full Adder

1. Full adders perform the arithmetic sum of three bits
2. Full adders is implemented by a 3-input 2-output combinational circuit
3. Truth Table:

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Binary Adder-Subtractor

■ K-Maps for Full Adders

 


Binary Adder-Subtractor

 ■ SOP Logic Implementations of Full Adders



Binary Adder-Subtractor

 ■ Full Adder Implementation with Two Half Adders and an OR Gate



Binary Adder-Subtractor

■ Binary Adders


1. Binary adders perform the arithmetic sum of two numbers
2. Binary adders can be constructed with full adders connected in cascade

Binary Adder-Subtractor

■ 4-bits Binary Adders


Subscript:	3	2	1	0	
Input Carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output Carry	0	0	1	1	C_{i+1}

4-bit Addition Example

 

Binary Adder-Subtractor


■ **n-bits Binary Adders**

 

Binary Adder-Subtractor

■ **Carry Propagation Delay:**

 
N-bit adder has 2n gate carry propagation delay !!



Binary Adder-Subtractor

■ **Carry Lookahead: Reduce Carry Propagation Delay**

 G_i : Carry Generate
 P_i : Carry Propagate




$$\begin{cases} P_i = A_i \oplus B_i \\ G_i = A_i B_i \end{cases} \rightarrow \begin{cases} S_i = P_i \oplus C_i \\ C_{i+1} = G_i + P_i C_i \end{cases}$$

Binary Adder-Subtractor


■ **Carry Lookahead: Carry Bits**

$C_0 = \text{Input Carry}$
 $C_1 = G_0 + P_0 C_0$
 $C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$
 $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

Binary Adder-Subtractor

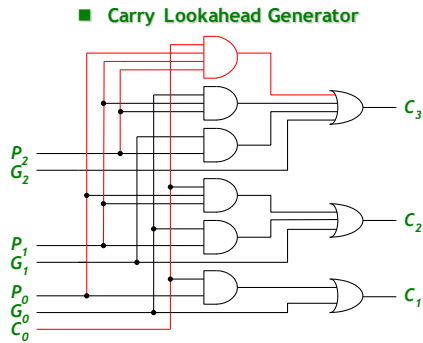


Binary Adder-Subtractor

 

Binary Adder-Subtractor

■ 4-bit Carry Lookahead Adder

 

Binary Adder-Subtractor

■ Binary Subtractor


1. Implement subtraction with 2's complement number system
2. $A - B = A + (-B) = A + 1'sc(B) + 1$
3. Implement 1'sc with XOR gates:

B	M	Output
0	0	0
0	1	1
1	0	1
1	1	0

Annotations:
 - Dashed arrow: 1'sc (Output = B) when M=0
 - Dotted arrow: 1'sc (Output = \bar{B}) when M=1

Binary Adder-Subtractor

4-Bit Binary Adder/Subtractor

 

Binary Adder-Subtractor

- Overflow:** When two numbers of n digits each are added and the sum occupies $n+1$ digits, we say that an overflow occurred.

8-bit 2'sc number presents [-128, +127]

