

Logic Families




Dept. of Computer Science and Engineering
 University of Rajshahi
 www.ru.ac.bd


Dr. Shamim Ahmad

- RTL - Resistor-Transistor Logic
- DTL - Diode-Transistor Logic
- TTL - Transistor-Transistor Logic
- ECL - Emitter-Coupled Logic
- MOS - Metal-oxide semiconductor
- CMOS - Complementary MOS


Diode based Logic

 

Diode based Logic

 

Diode based Logic

 


Bipolar Digital Gate Circuits

- The first forms of the digital ICs to receive general usage were BJT inverter circuits in earlier 1960s.
 - Circuits consisted of only resistors and transistors, - named *resistor-transistor logic (RTL)*.
- IC development a short time later consisted of a diode AND circuit followed a bipolar transistor inverter.
 - termed *diode-transistor logic (DTL)*


Transistor Based Logic

- Can use bipolar transistors

DTL

 


DTL

 

Resistor Transistor Logic

 - A diode AND network can be merged with an inverter
- Forms a diode-transistor NAND gate





Bipolar Digital Gate Circuits

- Choice of logic family for design of a specific digital system influenced by many factors.
 - Need for low power
 - High speed
 - Availability of more complex functions (MSI)
 - Compatibility with other parts of the system
 - cost
- Many system designs mix logic families
 - e.g. TTL and CMOS

- In the mid-late 1960's use of resistors, diodes and transistors began to disappear
 - Discrete components phased out due to new fabrication processes
 - Processes where entire circuits could be made onto one chip
- The first to appear were small scale integration SSI
 - 1 to 10 gates or memory elements packaged as a unit
 - packaged as DIL package
- MSI medium scale integration
 - 10 to 100 gates or memory elements packaged as a unit
- LSI large scale integration
 - 100 to 10000 gates or memory elements packaged as a unit
- For MSI and LSI the popular logic family is TTL


DTL NAND

  

DTL

The extra transistor adds amplification to increase fan-out

 
- kept in the active region when output transistor is saturated
- Modified circuit can supply large amount of base current to the output transistor.
- Thus output transistor can now draw a large



DTL


Part of the collector current comes from the conducting diodes in the loading gates (when the output transistor is saturated).

 - ⇒ an increase in allowable collector saturated current allows more loads to be connected to the output.
- ⇒ increase fan-out capability.




DTL

 - Extra diode is used to provide biasing for output transistor
- Avoids use of resistors
- and also the need for separate negative power supply




DTL -> TTL

 
- The first change from DTL to TTL:
 - In IC's it is easier to fabricate transistors than diodes.
 - When diodes are required transistors are used
 - ⇒ Usual to use the base-emitter junction of BJT
 - ∴ base serving as the anode
 - ∴ emitter serving as the cathode
 - ∴ collector tied to the base




TTL: NAND

 


TTL: NAND

 


TTL: NOR

 


TTL: NOR/NOT

 


TTL NOR gate implementation

 

TTL: Multi-Emitter Transistor

 


TTL AND gate implementation

 


TTL: Multi-Emitter Transistor

 - Note anodes of the input diodes are common
 - Thus can be realised in the form of a multiple-emitter transistor




TTL : Increase Switching Speed

 - The remaining changes in the evolution from DTL to TTL made to achieve increased speed.
- When circuit is to switch from a low-output to a highoutput state.
 - Q1 must go from saturation to cut-off
 - Requires removal of charge from base of Q1



TTL : Increase Switching Speed

 
- Therefore this switching action is brought about by Q2
 - Q2 going from saturation to cut-off
- The only path for discharging the base of Q1 through resistor R1.
- Speed of discharge is limited by time constant of circuit



TTL : Faster Switching

To obtain faster switching

 - Take advantage of input diodes being realised in terms of transistors
- change the circuit the following



How to increase speed ?

Whatever is done to the value of the resistors

- Speed is ultimately limited by the time required to pull the output transistors out of saturation.
 - many of the transistors, when conducting will be in a saturated condition
- 74, 74L and 74H series all operate with saturated switching
 - As has been seen this causes a saturation delay (storage delay), when switching from ON to OFF
 - limits the circuit's switching speed.





Schottky TTL, 74S series

- In Schottky TTL (STTL) • Transistors kept out of saturation by using Schottky barrier diodes (SD)
- Formed by a junction of a metal and semiconductor
 - conventional diode with a junction of *p*-type and *n*-type semiconductor material
 - SD connected between the base and the collector
 - Do not allow the transistors to go as deeply into saturation
 - SD has a forward voltage drop of 0.4V



Schottky TTL, 74S series

    - When the Collector-Base junction becomes forward biased at the on-set of saturation
 - ⇒ SD will conduct, diverting some input current away from base.
 - ⇒ this has effect of reducing the excess base current.
 - ⇒ decreases saturation (storage time) delay at turn-off
- 74S00 NAND has average propagation delay of 3 nsecs
 - twice as fast as the 74H00
 - makes the 74H series redundant nowadays



In output High condition

- Output High due to one of the inputs dropping low
 \Rightarrow Q3 and Q1 go into cut-off
- However output remains momentarily low
 - as voltage across load capacitance cannot change instantaneously

- As soon as Q₃ turns off
 \Rightarrow Q₂ conducts as its base is connected to V_{DD} via resistor.
- Current needed to charge load capacitance causes Q₂ to momentarily saturate
 \Rightarrow output voltage rises with a time constant RC


Transistor switches

- Logic circuits are built with transistors
- We will assume a transistor operates as a simple switch controlled by a logic signal x
- The most popular type of transistor for implementing a simple switch is the *metal oxide semiconductor field effect transistor* (MOSFET)
- Two types of MOSFETs
 - N-channel (*NMOS*)
 - P-channel (*PMOS*)
- Early circuits relied on NMOS or PMOS transistors, but not both
- Current circuits use both NMOS and PMOS transistors in a configuration called *complementary MOS* (CMOS)


Electrical & Computer Engineering

Dr. D. A. Jackson, Lecture 13-3

NMOS transistor as a switch

 


NMOS transistor as a switch

 


- The transistor operates by controlling the voltage V_G at the gate terminal
- If V_G is low, there is no connection between the source and the drain terminals. The transistor is **turned off**.
- If V_G is high, the transistor is **turned on** and acts as a closed switch between the source and drain terminals.

PMOS transistor as a switch

 


PMOS transistor as a switch

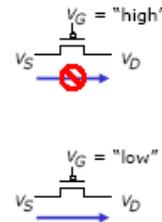

- The transistor operates by controlling the voltage V_G at the gate terminal
- If V_G is high, there is no connection between the source and the drain terminals. The transistor is **turned off**.
- If V_G is low, the transistor is **turned on** and acts as a closed switch between the source and drain terminals.

NMOS and PMOS in logic circuits

 


NMOS and PMOS in logic circuits

- When the NMOS transistor is turned on, its drain is **pulled down to Gnd**
- When the PMOS transistor is turned on, its drain is **pulled up to V_{DD}**
- Because of the way transistors operate:
 - An NMOS transistor cannot be used to pull its drain terminal completely up to V_{DD}
 - A PMOS transistor cannot be used to pull its drain terminal completely down to Gnd
- Therefore, NMOS and PMOS transistors are commonly used in pairs in CMOS circuits


CMOS logic gates

- A CMOS logic gate involves NMOS transistors in a **pull-down network** (PDN) and PMOS transistors in a **pull-up network** (PUN)
- The functions realized by the PDN and PUN networks are complements of one another
- The PDN and PUN have equal numbers of transistors, which are arranged so that the two networks are duals of one another
 - Wherever the PDN has NMOS transistors in series, the PUN has PMOS transistors in parallel, and vice versa


CMOS NOT gate

 


CMOS NAND gate

 

CMOS NOR gate

 


CMOS AND gate

 

6 transistors

CMOS OR gate

 

6 transistors
