



Dept. of Computer Science and Engineering
University of Rajshahi
www.ru.ac.bd

Dr. Shamim Ahmad


4 Basic types of Flip-Flops

- **SR, JK, D, and T**
- **JK** ff has
 - 2 inputs, J and K
 - Need to be asserted at the same time to change the state
- **D** ff has
 - 1 input D (DATA)
 - Which sets the ff when $D = 1$ and resets it when $D = 0$


4 Basic types of Flip-Flops

- **T** ff has
 - 1 input T (Toggle)
 - Which forces the ff to change states when $T = 1$
- **SR** ff has
 - 2 inputs, S (set) and R (reset)
 - That set or reset the output Q when asserted

SR FF (active HIGH)

 


(a) Active-HIGH input S-R latch


 


(a) Active-HIGH input S-R latch


SR FF NOR gate

 


SR FF (active LOW)

  

SR FF (NAND gate)

 


S_L	R_L	Q	QN
0	0	1	1
0	1	1	0
1	0	0	1
1	1	last Q	last QN

 


SR FF Truth Table

INPUTS		OUTPUTS		COMMENTS
\bar{S}	\bar{R}	Q	\bar{Q}	
1	1	NC	NC	No change. Latch remains in present state.
0	1	1	0	Latch SET.
1	0	0	1	Latch RESET.
0	0	1	1	Invalid condition


SR FF with Enable input

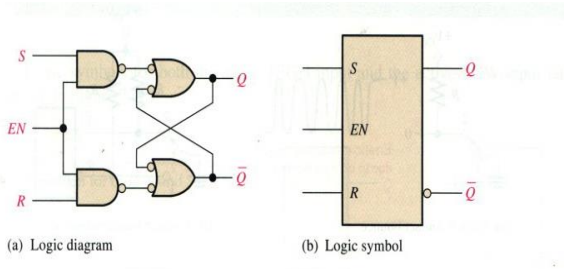

The Gated S-R Latch

 


Edged-Triggered S-R FF

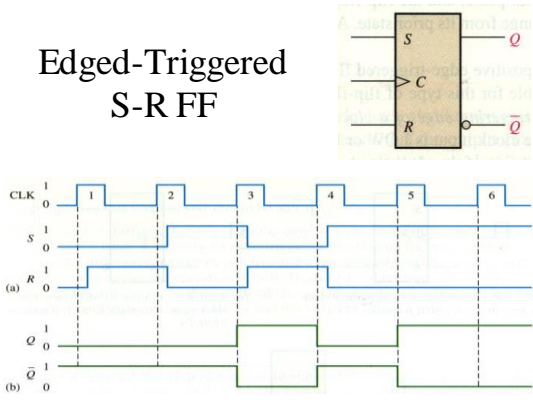


Clocked D Flip-Flop

 - Clocked D Flip-Flop.**
- Output follows D input while clock is 1.
 - Output is remembered while clock is 0.




Gated D-Latch

 


- Ensures S and R inputs never equal to 1 at the same time
- Useful in control application where setting or resetting a flag to some condition is needed
- Stores bits of information
- Constructed from a gated SR latch and a Data latch


The Gated D Latch

 


Positive edge-triggered D FF

 


The Gated D Latch

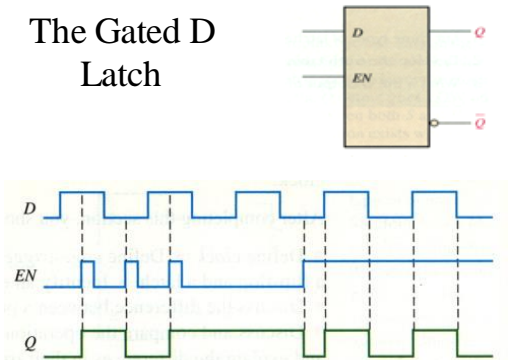

JK flip-flop timing diagram

 

Edge-Triggered D FF

 


INPUTS		OUTPUTS		COMMENTS
D	CLK	Q	\bar{Q}	
1	↑	1	0	SET (stores a 1)
0	↑	0	1	RESET (stores a 0)

↑ = clock transition LOW to HIGH

TABLE 7-3
Truth table for a positive edge-triggered D flip-flop.


Edge-Triggered D FF

 


Edge-Triggered JK-FF

- JK-FF is versatile and is a widely used type of flip-flop.
- The functioning of the JK-FF is identical to that of the SR-FF in the SET, RESET, and NC.
 - The **difference** is that the JK-FF **has NO invalid state** as does the SR-FF.


Edge-Triggered JK-FF

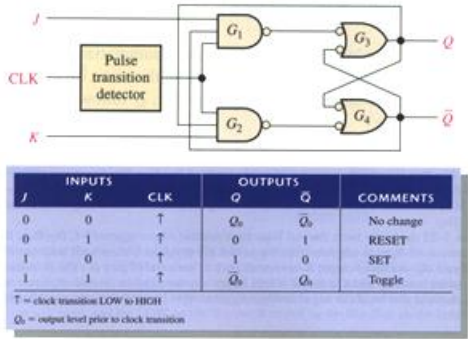

Edge-Triggered JK-FF

 


Edge-Triggered JK-FF

 


Edge-Triggered J-K flip-flop

J	K	CLK	Q	QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN
0	0	↑	last Q	last QN
0	1	↑	0	1
1	0	↑	1	0
1	1	↑	last QN	last Q

 


Asynchronous Preset and Clear Inputs

 - Most IC flip-flops have **asynchronous** inputs.
 - These are inputs that affect the state of the FF **independent of the clock**.
 - Preset (PRE) or direct set (S_D)
 - Clear (CLR) or direct reset (R_D)




Edge-triggered JK-FF with PRE and CLR

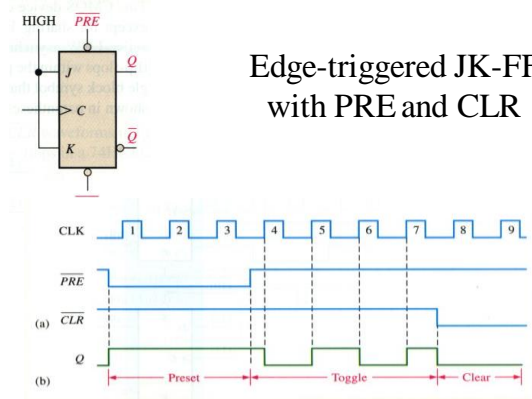

Master/slave J-K flip-flop (Pulse triggered)

J	K	C	Q	QN
x	x	0	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		last QN	last Q

 

T flip-flop

- The name T derives from the behavior of the circuit, which 'toggles' its state when $T=1$
 - This feature makes the T flip-flop a useful element when constructing counter circuits

