
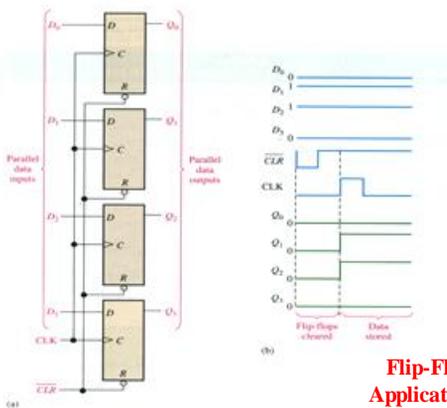


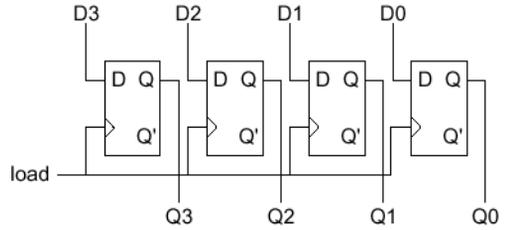

Dept. of Computer Science and Engineering
 University of Rajshahi
 www.ru.ac.bd
 Dr. Shamim Ahmad

Flip-Flop Applications

Register




Flip-Flop Applications

Flip-Flop Applications

► **FIGURE 7-37**
 The J-K flip-flop as a divide-by-2 device. Q is one-half the frequency of CLK.

Frequency division

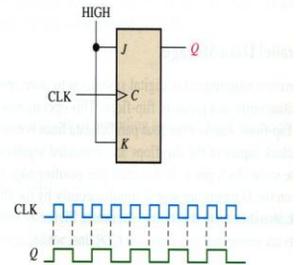

Flip-Flop Applications



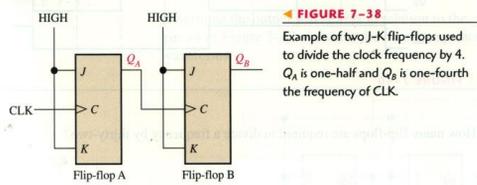
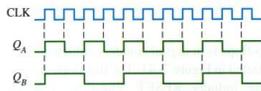


FIGURE 7-38
 Example of two J-K flip-flops used to divide the clock frequency by 4. Q_A is one-half and Q_B is one-fourth the frequency of CLK.

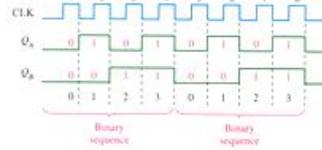


Frequency division

Flip-Flop Applications


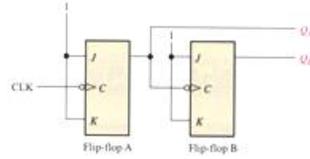


Counting

Flip-Flop Applications

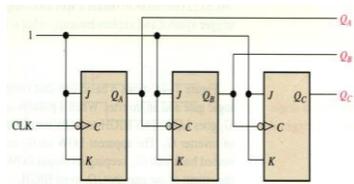


Counting

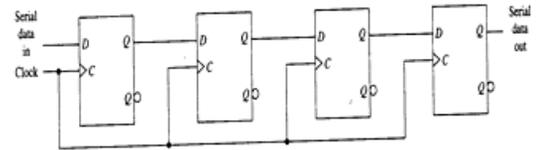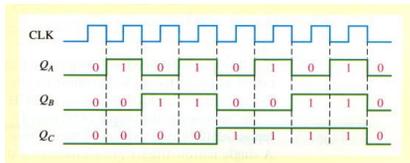


- ❑ Register is a group of Flip-Flops.
- ❑ It stores binary information 0 or 1.
- ❑ It is capable of moving data left or right with clock pulse.
- ❑ Registers are classified as



Shift Register

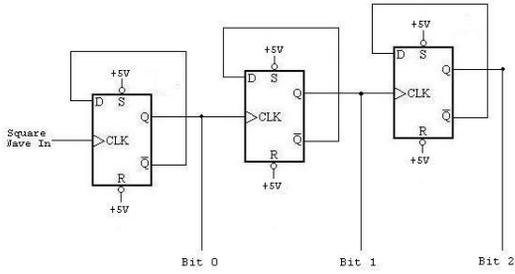


Shift Register

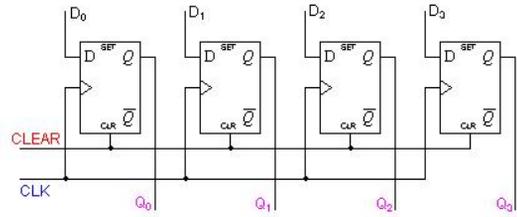

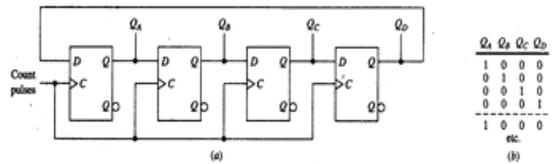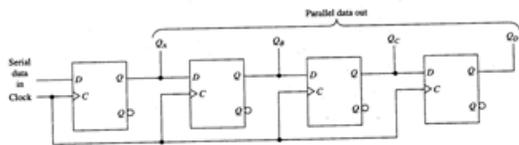
- Parallel-in Serial-Out
- Parallel-in parallel Out



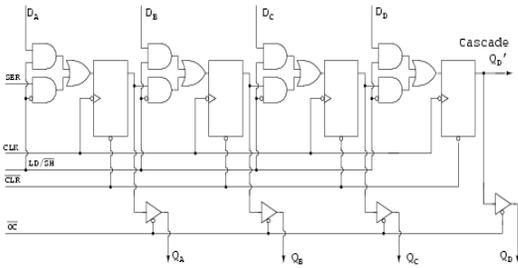
- ❑ The output of LSB FF is connected as D input to MSB FF.
- ❑ This is commonly called as Ring Counter or Circular Counter.
- ❑ The data is shifted to right with each clock pulse.
- ❑ This counter has four different states.
- ❑ This can be extended to any no. of bits.



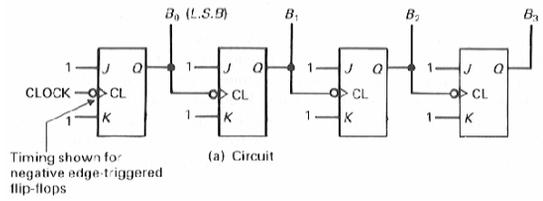
74LS395 parallel-in/ parallel-out shift register with tri-state output




(a) Circuit

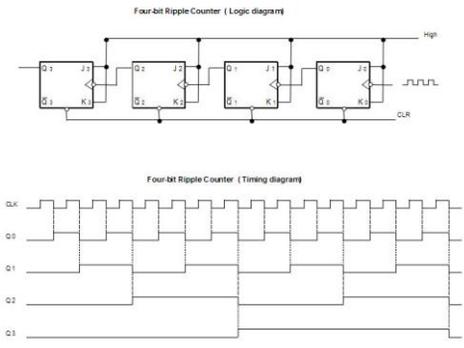


Counter

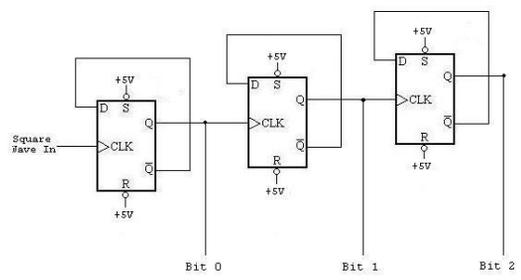


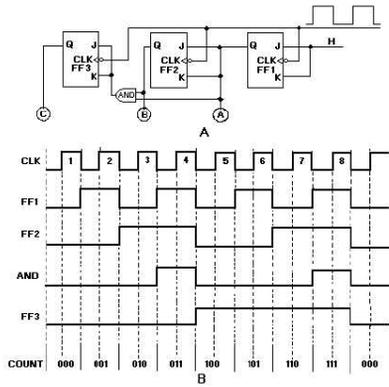


Twisted Ring Counter or Johnson Counter

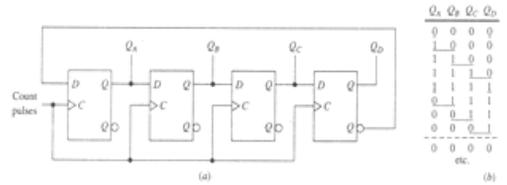


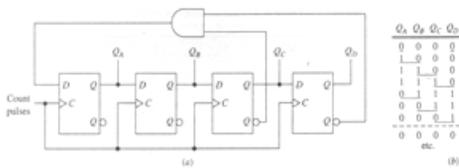
- ❑ The complement output of LSB FF is connected as D input to MSB FF.
- ❑ This is commonly called as Johnson Counter.
- ❑ The data is shifted to right with each clock pulse.
- ❑ This counter has eight different states.
- ❑ This can be extended to any no. of bits.




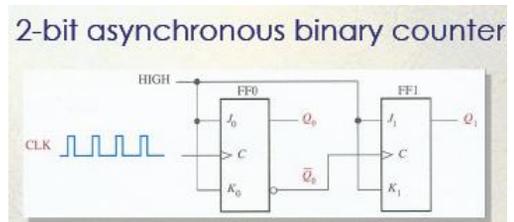
- ❑ The D input to MSB FF is
- ❑ The counter follows seven different states with application of clock input.
- ❑ By changing feedback different counters can be obtained.




3-Bit Up/Down Synchronous Counter

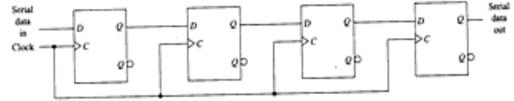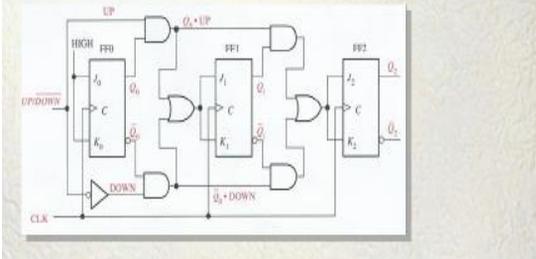

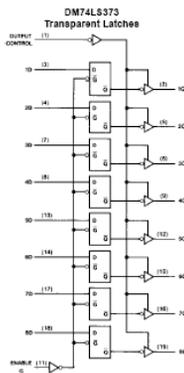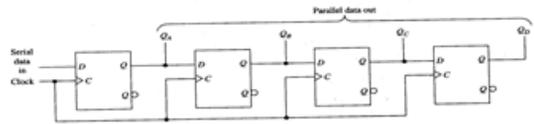- ❑ Register is a group of Flip-Flops.
- ❑ It stores binary information 0 or 1.
- ❑ It is capable of moving data left or right with clock pulse.
- ❑ Registers are classified as



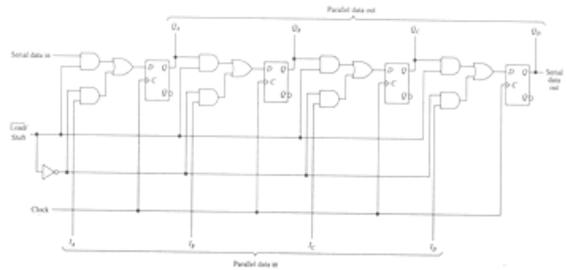
Parallel-in Unidirectional Shift Register



- ❑ Parallel input data is applied at $I_A I_B I_C I_D$.
- ❑ Parallel output $Q_A Q_B Q_C Q_D$.
- ❑ Serial input data is applied to A FF.
- ❑ Serial output data is at output of D FF.
- ❑ L/Shift is common control input.
- ❑ $L/S = 0$, Loads parallel data into register.
- ❑ $L/S = 1$, shifts the data in one direction.


Select lines		Register operation
S_1	S_0	
0	0	Hold
0	1	Shift right
1	0	Shift left
1	1	Parallel load

Universal Shift Register

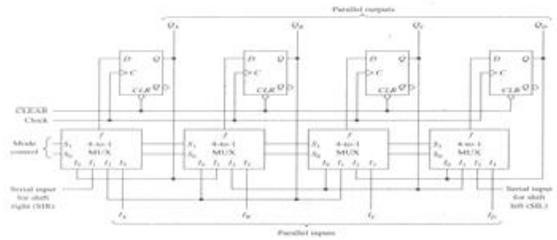


- Bidirectional Shifting.
- Parallel Input Loading.
- Serial-Input and Serial-Output.
- Parallel-Input and Serial-Output.
- Common Reset Input.
- 4:1 Multiplexer is used to select register operation.

Synchronous Binary Counter

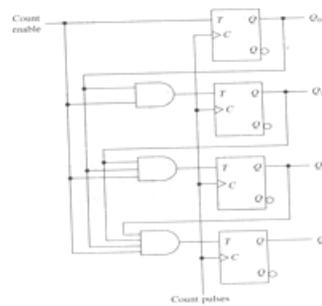

- ❑ The clock input is common to all Flip-Flops.
- ❑ The T input is function of the output of previous flip-flop.
- ❑ Extra combination circuit is required for flip-flop input.

Counters Based on Shift Register

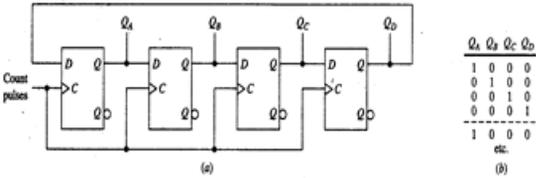

- The output of LSB FF is connected as D input to MSB FF.
- This is commonly called as Ring Counter or Circular Counter.
- The data is shifted to right with each clock pulse.
- This counter has four different states.
- This can be extended to any no. of bits.