 


# Parasitics & Delay Calculation


# Parasitics and Performance

- Consider the following layout:
- What is the impact on performance of parasitics
  - ☞ At point a (VDD rail)?
  - ☞ At point b (input)?
  - ☞ At Point c (output)?



 
# Parasitics and Performance

- a - power supply connections
  - ☞ capacitance - no effect on delay
  - ☞ resistance - increases delay (see p. 135)
    - ⊖ minimize by reducing diffusion length
    - ⊖ minimize using parallel vias


 
# Parasitics and Performance


- b - gate input
  - ☞ capacitance increases delay on previous stage (often transistor gates dominate)
  - ☞ resistance increases delay on previous stage



## Parasitics and Performance
 
### c - gate output


- ∞ resistance, capacitance increase delay
- ∞ Resistance & capacitance "near" to output causes additional delay




## Delay

Delay in VLSI refers to the **time** taken for a signal to propagate through a circuit. They describe various types of delays, including *cell delay*, *net delay*, and *propagation delay*, as well as related concepts like rise time and fall time.

## Ways of measuring gate delay

 

 
- **Delay**: time required for gate's output to reach 50% of final value.
- **Transition time**: time required for gate's output to reach 10% (logic 0) or 90% (logic 1) of final value.



$t_r$  = Rise transition time  
 $t_f$  = Fall transition time  
 $t_{pLH}$  = Propagation delay high-low  
 $t_{pHL}$  = Propagation delay low-high
 
## Inverter Delay

It is necessary to take the load into account in even the simplest inverter delay analysis. **The load on the inverter is a single resistor-capacitor (RC) circuit; the resistance and capacitance come from the logic gate connected to the inverter's output and the wire connecting the two.**



## Delay assumptions


- Assume that only one transistor is on at a time. This gives two cases:
  - rise time, pullup on;
  - fall time, pullup off.
- Assume resistor model for transistor. Ignores saturation region and mischaracterizes linear region, but results are acceptable.

## Delay Model

- $\lambda$  model : Mead & Conway
- Current source model
- Fitted Model
 
## Current through transistor

- Transistor starts in saturation region, then moves to linear region.



## Capacitive Load

- **Unit load capacitance**  $C_l$  as 1/2 of the load capacitance of a minimum-size inverter driving another minimum-size inverter.
- $C_l$  includes all the capacitances of the load transistors as well as the capacitances of the driving transistors that affect that node. In 80nm process  $C_l = 0.89 fF$ .


load capacitance  $C_L$  presented by another gate with different function and transistor sizes, we scale each transistor in the gate appropriately based on the transistor sizes

$$C_L = \sum_{1 \leq i \leq n} \frac{W}{L_i} C_l$$

## Resistive model for transistor

- Average  $V/I$  at two voltages:
  - maximum output voltage
  - middle of linear region
- Voltage is  $V_{ds}$ , current is given  $I_d$  at that drain voltage. Step input means that  $V_{gs} = V_{DD}$  always.

## Resistive approximation

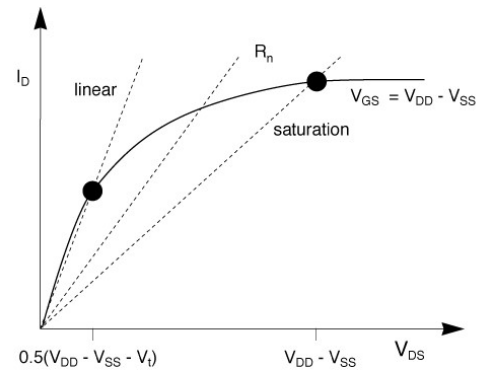

## Transistor's Effective Resistance


The table shows the effective resistance values for **minimum-size n-type and p-type** transistors in **180 nm** process. The effective resistance of a transistor is scaled by  $L/W$ :

type	$V_{DD}-V_{SS} = 1.2V$
$R_n$	6.47 k $\Omega$
$R_p$	29.6 k $\Omega$


$$R_t = \frac{W}{L} R_{n,p}$$
 
## Inverter delay circuit


- Load is resistor + capacitor, driver is resistor.



## Delay of a Minimum-Size Inverter

 

 $R$  = Average 'ON' resistance of transistor  
 $C$  = Output Capacitance



To find 't' at  $V_{dd}/2$ .  
 $V_{out} = (1 - e^{-t/\tau})V_{dd}$   
 $\tau = RC = \text{time constant}$   
 Substituting ' $V_{out}$ ' equal to  $V_{dd}/2$ , and 't' equal to ' $t_p$ '  
 $V_{dd}/2 = (1 - e^{-t_p/\tau}) V_{dd}$   
 $t_p = \ln(2) \tau = 0.69\tau$

Propagation delay = 50% of input to 50% of output

## Inverter delay with $\tau$ model

- $\tau$  model: gate delay based on RC time constant  $\tau$ .
- $V_{out}(t) = V_{DD} \exp\{-t/(R_n + R_L)/C_L\}$
- $t_f = 2.2 R C_L$
- For pullup time, use pullup resistance.