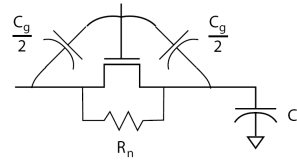


Topics


- Switch Logic
- Pseudo-nMOS gates.
- DCVS logic.
- Domino gates.

n-type Switch



- It requires only one transistor and one gate signal. It transmits a logic 0 well, but when V_{DD} is applied to the drain, the voltage at the source is $(V_{DD} - V_{in})$.
- When switch logic drives gate logic, n-type switches can cause electrical problems.


Transmission gate

 

- when V_{DD} or V_{SS} is applied to the drain, V_{DD} or V_{SS} appears at the source.
- It requires
 - two transistors and their associated tubs;
 - both true and complement forms of the gate signal

Pseudo-nMOS

 - Uses a p-type as a resistive pullup, n-type network for pulldowns.



Characteristics

- Consumes static power.
- Has much smaller pullup network than static gate.
- Pulldown time is longer because pullup is fighting.

Output voltages

- Logic 1 output is always at V_{DD} .
- Logic 0 output is above V_{SS} .
- $V_{OL} = 0.25 (V_{DD} - V_{SS})$ is one plausible choice.

Producing output voltages

- For logic 0 output, pullup and pulldown form a voltage divider.
- Must choose n, p transistor sizes to create effective resistances of the required ratio.
- Effective resistance of pulldown network must be computed in worst case—series n-types means larger transistors.

Transistor ratio calculation

- In steady state logic 0 output:
 - pullup is in linear region, $V_{ds} = V_{out} - (V_{DD} - V_{SS})$;
 - pulldown is in saturation.
- Pullup and pulldown have same current flowing through them.


Transistor ratio, cont'd.

- Equate two currents:

$$-I_{dp} = I_{dn}$$

- Using 0.5 μm parameters, 3.3V power supply:


$$-W_p/L_p / W_n/L_n = 3.9.$$

 

DCVS logic

- DCVSL = differential cascode voltage logic.
- Static logic—consumes no dynamic power.
- Uses latch to compute output quickly.
- Requires true/complement inputs, produces true/complement outputs.


DCVS structure

 

DCVS operation

- Exactly one of true/complement pulldown networks will complete a path to the power supply.
- Pulldown network will lower output voltage, turning on other p-type, which also turns off p-type for node which is going down.

DCVS example

 

Modern VLSI Design 4c: Chapter 3

Copyright © 2008 Wayne Wolf

Other low-power gates

- The simplest way to reduce the operating voltage of a gate is to connect it to a lower power supply. We saw the relationship between power supply voltage and power consumption in Section 3.3.5:

- For large V_p , Equation 3-7 tells us that delay changes linearly with power supply voltage.


$$t_f = \frac{C_L(V_{DD}-V_{SS})}{I_d} = \frac{C_L(V_{DD}-V_{SS})}{0.5K(W/L)(V_{DD}-V_{SS}-V_t)^2} \quad (\text{EQ 3-7})$$

- Equation 3-15 tells us that power consumption varies quadratically with power supply voltage.


Modern VLSI Design 4c: Chapter 3

Copyright © 2008 Wayne Wolf

Delay in Wires: Lumped RC Model

 

Lumped RC Model:

 

$$\begin{aligned} R &= R_s \cdot L / W = r \cdot L \\ (r &= R_s / W - \text{resistance per unit length}) \\ C &= L \cdot W \cdot C_{\text{plate}} = c \cdot L \\ (c &= W \cdot C_{\text{plate}} - \text{capacitance per unit length}) \end{aligned}$$

- Delay time constant (ignoring driving gate)

$$\begin{aligned} \tau &= R \cdot C = (R_s \cdot L / W) \cdot (L \cdot W \cdot C_{\text{plate}}) \\ &= r \cdot c \cdot L^2 \end{aligned}$$


- Problem: Overly Pessimistic

Modern VLSI Design 4c: Chapter 3

Copyright © 2008 Wayne Wolf

Delay in Long Wires - Distributed RC Model

 - Alternative: Break wire into small segments



- Approx. Solution - 1st moment of impulse response

$$\tau(V_{\text{out}}) = rc(\Delta L)^2 \left(\frac{N(N+1)}{2} \right)$$

$$\tau(V_{\text{out}}) = \frac{rcL^2}{2} \quad \text{for } N \rightarrow \infty$$

- Important: delay still grows as square of length

Modern VLSI Design 4c: Chapter 3

Copyright © 2008 Wayne Wolf


Delay in Long Wires - Consequences in design

■ Distributed RC model:




■ Delay grows as square of L !

 - Choose wire material that minimizes r , c
- Break wire into buffered segments to optimize delay



Elmore Delay

 ■ Consider R-C ladder network with unequal values



■ First-order time constant at node N is

$$\tau_N = \sum_{i=1}^N R_i \sum_{j=i}^N C_j = \sum_{i=1}^N C_i \sum_{j=1}^i R_j$$

■ First-order time constant and node I is


$$\tau_i = C_1 R_1 + C_2 (R_1 + R_2) + \dots + C_i (R_1 + R_2 + \dots + R_i)$$

Elmore Delay Applications

- Wire sizing to minimize delay
- Delay prediction of complex networks (as long as they take the form of a ladder)

Wire Sizing

 ■ Recall distributed model of wire: multiple segments




$$\tau_i = C_1 R_1 + C_2 (R_1 + R_2) + \dots + C_i (R_1 + R_2 + \dots + R_i)$$

note strong impact of R_1 , lesser impact of R_2 , etc

- Idea: Reduce overall delay by tapering segments
 - Make Segment 1 widest to reduce R_1 (increases C_1)
 - Make Segment 2 less wide to reduce R_2 (increases C_2)
 - etc.

Wire Sizing

 - Ideal Result wire should taper exponentially - see Eq. 3-20, p. 163 [Fis95]:




More pragmatic approach: step-tapered wire



[Fis95] J. Fishburn and C. Schevon, "Shaping a distributed-RC line to minimize Elmore delay", *IEEE Trans. on Circuits and Systems-I*, December 1995, pp. 1020-1022


Delay in RC-Trees

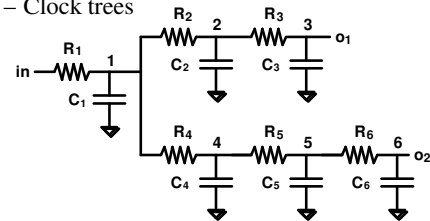- Many interconnection networks are trees
 - Extracted RC circuit modeling a gate output
 - Clock trees



Delay in RC-Trees: Penfield-Rubenstein Bounds

 - Key idea: characterize time constants in terms of
 - Path resistances between nodes
$$R_{k0} = \sum R_j \Rightarrow (R_j \in [\text{path}(\text{in} \rightarrow o) \cap \text{path}(k \rightarrow o)])$$
- Capacitance values at each node



Elmore Delay Problem

- What are the Elmore time constants τ_1 , τ_2 , τ_3 ?

